



Finite Element Models for Eddy Current Effects in Windings: Application to Superconductive Rutherford Cable

Herbert De Gersem^{1←2}, Thomas Weiland¹

¹Technische Universität Darmstadt (Germany),
Computational Electromagnetics Laboratory

²Katholieke Universiteit Leuven (Belgium)
Dep. ESAT, Div. ELECTA

MACSI-NET-13 & 2: “Electromagnetics in Telecommunication”
Workshop “Coupled problems / model reduction”
2-3 May 2003, Zürich, Switzerland

1. Introduction: field-circuit coupling
2. Voltage/current-driven branches
3. Circuit description
 - + consistency check
 - + partial loop/cutset transformations
 - + topological changes
4. Field-circuit coupling
 - + examples
5. Algebraic system properties
 - + selection of iterative solution techniques
6. Superconductive Rutherford cable
 - + adjacency eddy currents
 - + cross-over eddy currents
7. Conclusions


field-circuit coupling

FE/FIT model

- geometrical details
- ferromagnetic saturation (non-linear!!)
- (motional) eddy currents

circuit

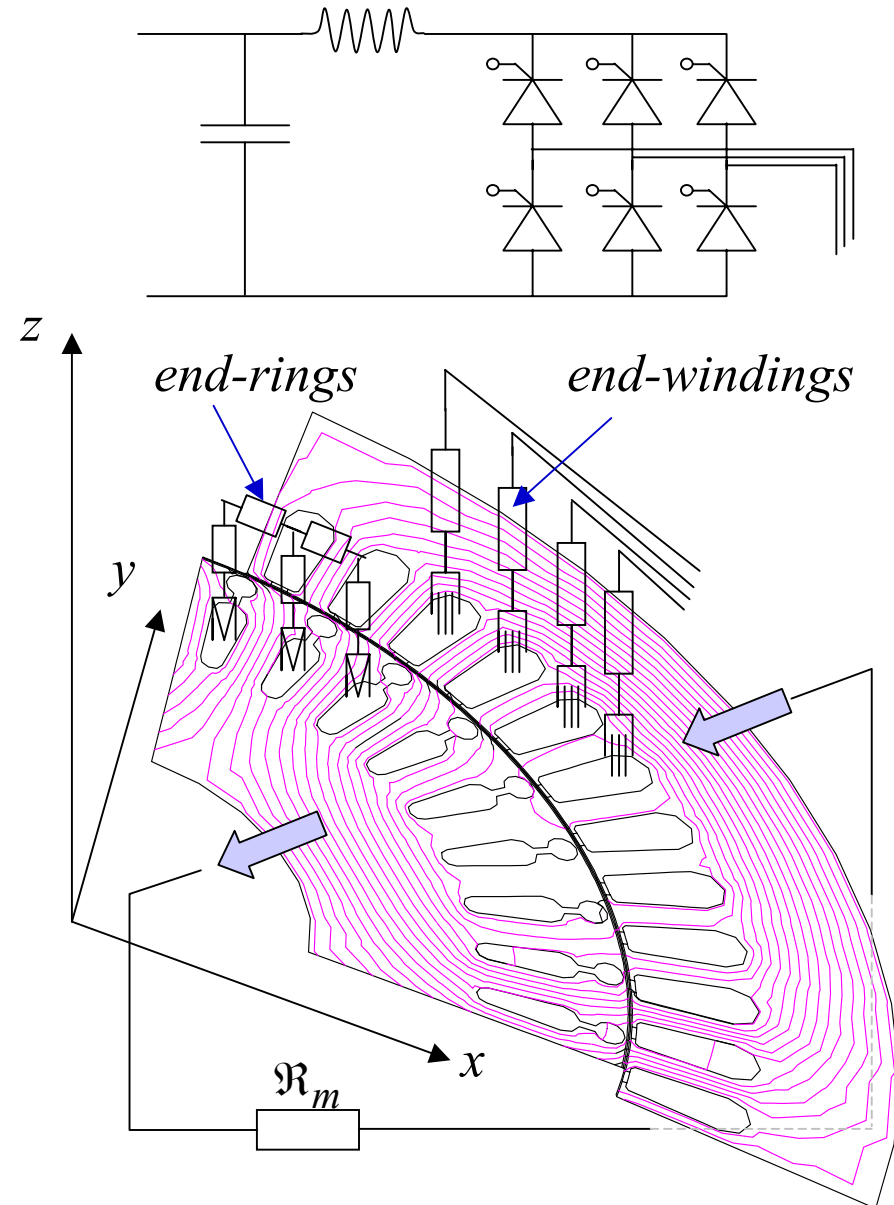- external sources/loads, (e.g. power electronic equipment)
- parts outside the FE model (e.g. end windings/rings)
- representing (linear) parts for which an equivalent circuit suffices (e.g. homopolar shaft flux)



Quasistatic formulation

magnetic vector potential pulsation

$\mathbf{B} = \nabla \times \mathbf{A}$

velocity

voltage


$$\nabla \times (\mathbf{v} \nabla \times \mathbf{A}) - \sigma \mathbf{v} \times (\nabla \times \mathbf{A}) + j\omega \sigma \mathbf{A} + \sigma \frac{\partial \mathbf{A}}{\partial t} = -\sigma \nabla V$$

reluctivity

conductivity

2D model

$\mathbf{A} = (0, 0, A_z)$

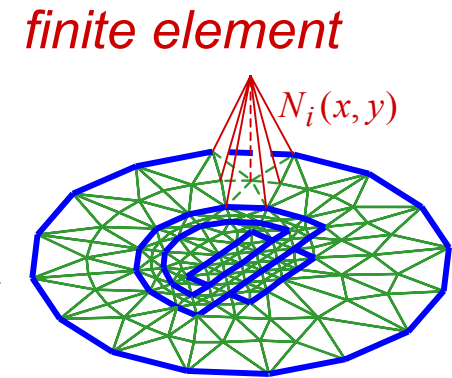

$$-\frac{\partial}{\partial x} \left(\mathbf{v} \frac{\partial A_z}{\partial x} \right) - \frac{\partial}{\partial y} \left(\mathbf{v} \frac{\partial A_z}{\partial y} \right) + \sigma v_x \frac{\partial A_z}{\partial x} + \sigma v_y \frac{\partial A_z}{\partial y} + j\omega \sigma A_z + \sigma \frac{\partial A_z}{\partial t} = \frac{\sigma}{l_z} V$$

discretisation


$$A_z = \sum_j A_{z,j} N_j(x, y)$$

$$k_{ij} = \int_{\Omega} \mathbf{v} \left(\frac{\partial N_i}{\partial x} \frac{\partial N_j}{\partial x} + \frac{\partial N_i}{\partial y} \frac{\partial N_j}{\partial y} \right) d\Omega$$

$$\underbrace{[k_{ij} + m_{ij} + l_{ij}]} [A_{z,j}] = [f_i]$$

large & sparse system of equations

Solid (massive) conductor

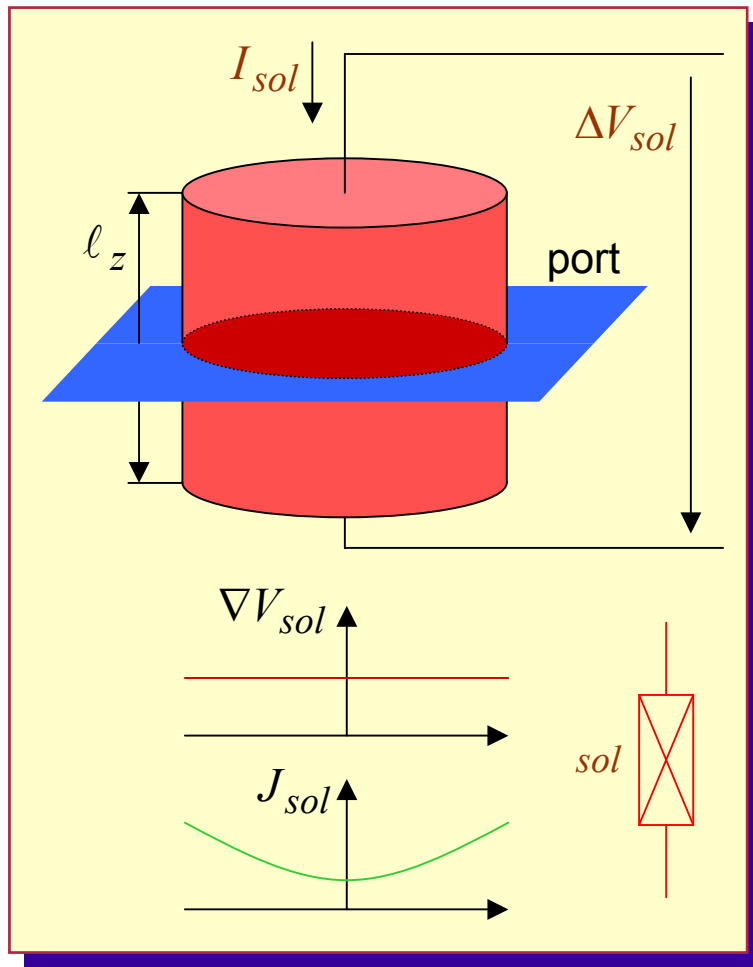

“voltage-driven” conductor

no circuit equation if voltage drop is known
no fill-in in the FE matrix part if the voltage drop is an independent degree of freedom

- magnetic equation


$$\nabla \times (\nu \nabla \times \mathbf{A}) + \sigma \frac{\partial \mathbf{A}}{\partial t} = \frac{\sigma}{l_z} \Delta V_{sol}$$

- total current $I_{sol} = \int_{\Omega_{sol}} \mathbf{J} d\Omega$


$$I_{sol} = \underbrace{\int_{\Omega_{sol}} \frac{\sigma}{l_z} d\Omega \Delta V_{sol}}_{G_{sol}} - \underbrace{\int_{\Omega_{sol}} \sigma \frac{\partial \mathbf{A}}{\partial t} d\Omega}_{I_{eddy}}$$

$I_{source} \qquad I_{eddy}$

- equivalent scheme

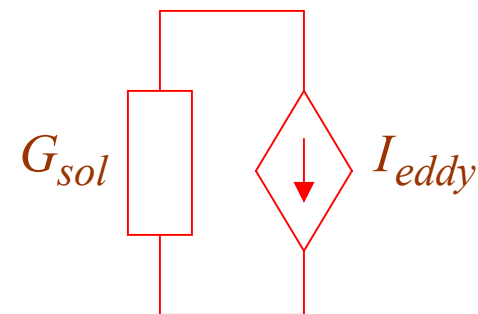

Stranded (filamentary) conductor

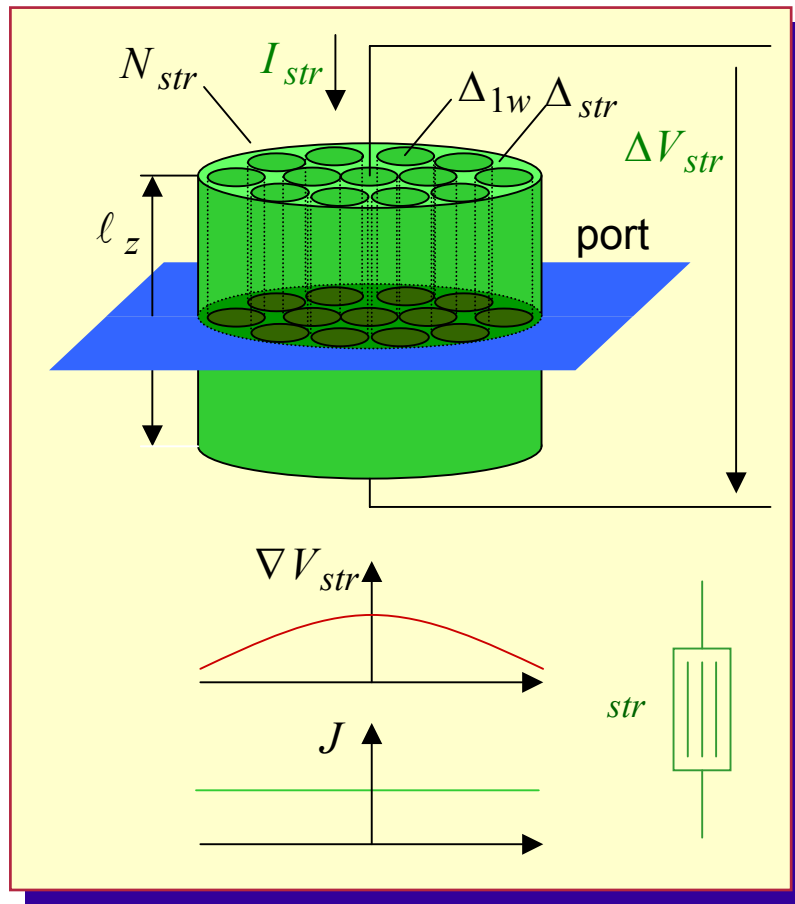

“current-driven” conductor

no circuit equation if current is known
no fill-in in the FE matrix part if the current is an independent degree of freedom

- magnetic equation


$$\nabla \times (\nu \nabla \times \mathbf{A}) = \frac{N_{str}}{\Delta_{str}} I_{str}$$

- total voltage

$$\Delta V_{str} = \frac{N_{str} \ell_z}{\Delta_{str}} \int_{\Omega_{str}} (-\nabla V) d\Omega$$

$$\Delta V_{str} = \underbrace{R_{str} I_{str}}_{\Delta V_{res}} + \underbrace{\frac{N_{str} \ell_z}{\Delta_{str}} \int_{\Omega_{str}} \frac{\partial \mathbf{A}}{\partial t} d\Omega}_{\Delta V_{ind}}$$

- equivalent scheme

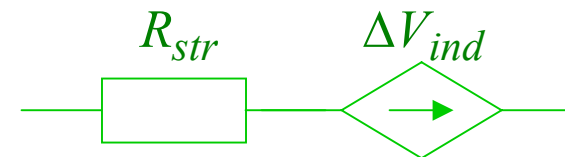

Coupling requirements

$$\begin{bmatrix} K & B^T \\ B & C \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} f \\ g \end{bmatrix}$$

*(compacted)
modified
nodal analysis*

*(compacted)
loop analysis*

*hybrid
analysis*

unknowns

*nodal voltages
(+a few currents)*

*loop currents
(+a few voltages)*

*twig voltages
link currents*

*keep the FE matrix part
unchanged*

- sparsity
- preconditioners (multigrid)
- possible benefits thanks to structured grids (FIT)

no (yes)

no (yes)

yes

preserve symmetry

- Krylov subspace solvers for symmetric systems (CG, MINRES, QMR)

yes

yes

yes

- storage

preserve positive definiteness

- solvers (CG)
- preconditioners (IC)


yes (no)

yes (no)

no [yes]

Circuit description (1)

1. Trace a tree through the circuit

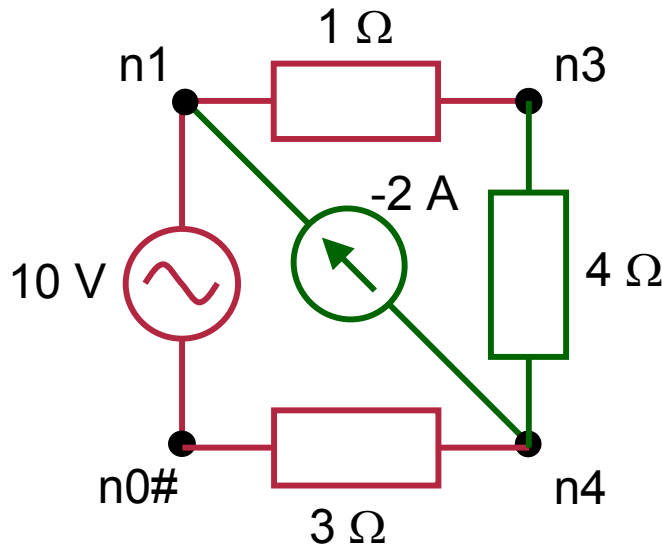

— twig
— link

starting from the circuit node n0#,
the twigs are selected in the order

1. voltage source 10 V
2. resistor 1 Ω
3. resistor 3 Ω

Priority list

highest priority, preferably **twig**

voltage sources

solid conductors (coupled)

capacitors (largest capacitance first)

resistors (largest conductance first)

inductors (smallest inductance first)


stranded conductors (coupled)

current sources

smallest priority, preferably **link**

Circuit description (2)

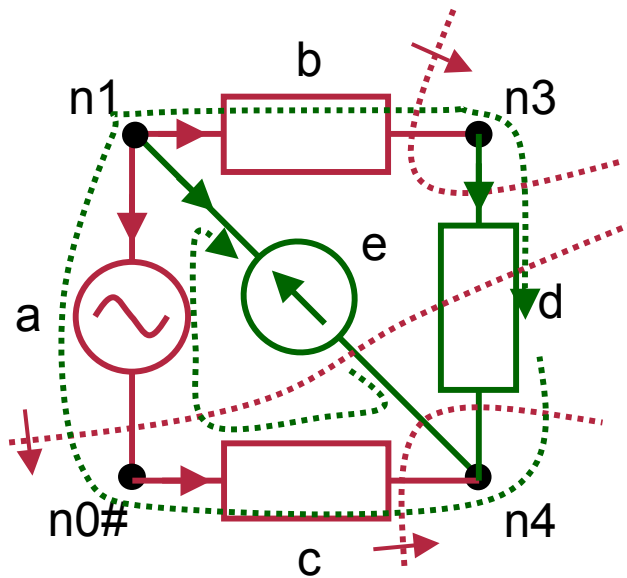2. Determine fundamental cutsets and fundamental loops



..... fundamental cutset
 fundamental loop

The orientation of the fundamental **cutset**/**loop** is determined by the orientation of the corresponding **twig**/**link**

A **fundamental cutset** is formed by 1 **twig** and the unique set of links completing the set of branches which would upon removal result in two disconnected circuit parts.


A **fundamental loop** consists of 1 **link** and the unique path through the tree closing the loop.

Property: $\text{priority}(\text{twig}) \geq \text{priority}(\text{branch}),$
 $\forall \text{branch} \in \text{fundamental cutset}$

Property: $\text{priority}(\text{link}) \leq \text{priority}(\text{branch}),$
 $\forall \text{branch} \in \text{fundamental loop}$

Circuit description (3)

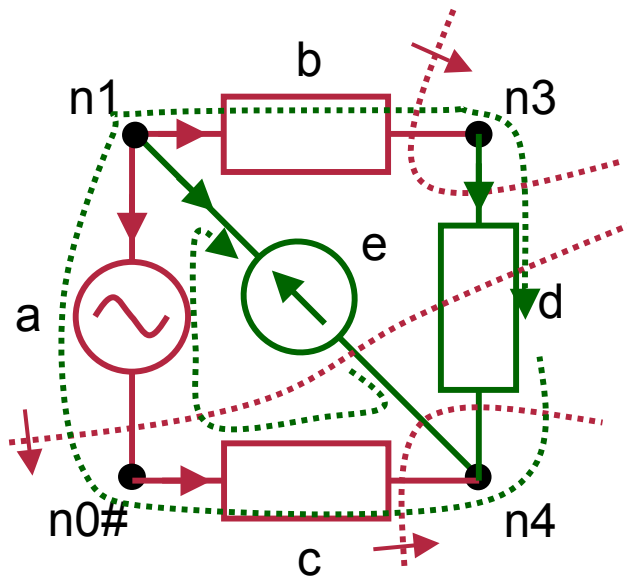3. Construct the fundamental cutset and fundamental loop matrices



fundamental cutset matrix

$$D = \left[\begin{array}{ccc|cc} 1 & & & 1 & 1 \\ & 1 & & -1 & \\ & & 1 & 1 & 1 \end{array} \right]$$


fundamental loop matrix

$$B = \left[\begin{array}{ccc|c} -1 & 1 & -1 & 1 \\ -1 & & -1 & 1 \end{array} \right]$$

remark: $B_{ln,tw} = -D_{tw,ln}^T$

Circuit description (4)

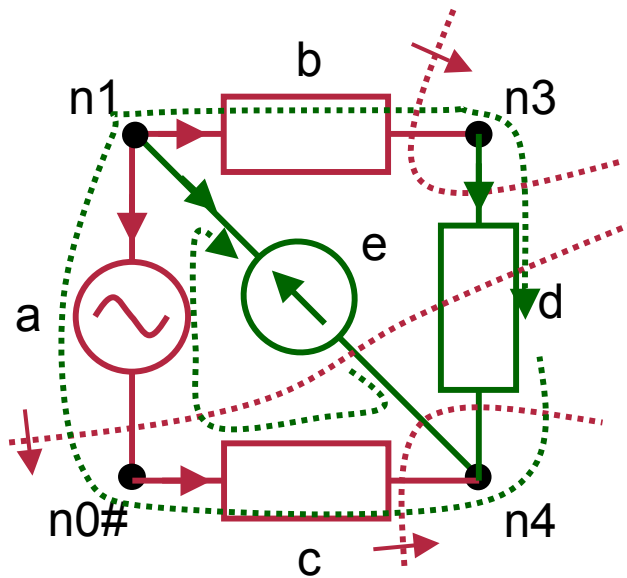4. Partition the fundamental incidence matrices



$$D = \begin{bmatrix} 1 & & & & \\ & 1 & & & \\ & & 1 & & \\ & & & 1 & \\ & & & & 1 \end{bmatrix}$$


$\begin{bmatrix} 1 & 1 \\ -1 & \\ 1 & 1 \end{bmatrix}$

$D_{twv, lno}$
 $D_{twv, lni}$
 $D_{two, lni}$
 $D_{two, lno}$

twv	twigs at which the voltage is known (voltage sources)
two	twigs at which an unknown voltage is assigned (" <i>free twigs</i> ")
twu	eliminated twigs (" <i>eliminated twigs</i> ") (not in this example)
lnu	eliminated links (" <i>eliminated links</i> ") (not in this example)
lno	links at which an unknown current is assigned (" <i>free links</i> ")
lni	links at which the current is known (current sources)

Circuit description (5)

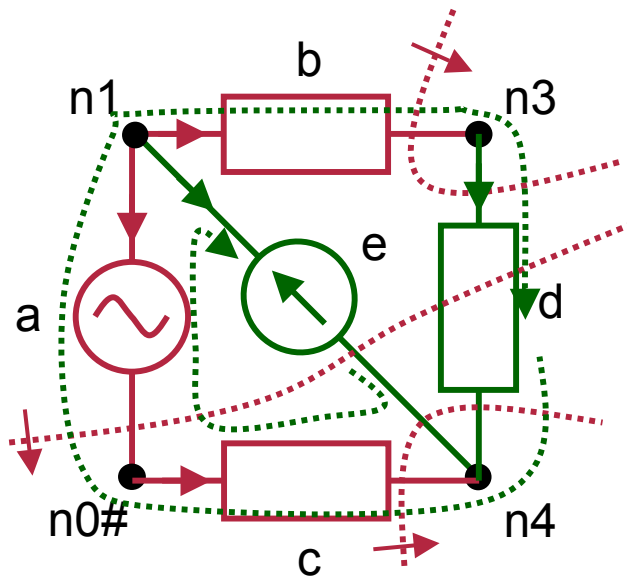5. Write impedance/admittance matrices and voltage/current vectors



1. admittance matrix for the free twigs

$$Y_{\text{two}} = \begin{bmatrix} 1/1 & \\ & 1/3 \end{bmatrix}$$

2. impedance matrix for the free links

$$Z_{\text{lno}} = [4]$$

3. voltage vector for the voltage sources


$$v_{\text{twv}} = [10]$$

4. current vector for the current sources

$$i_{\text{lni}} = [2]$$

Circuit description (6)

6. Write system of equations

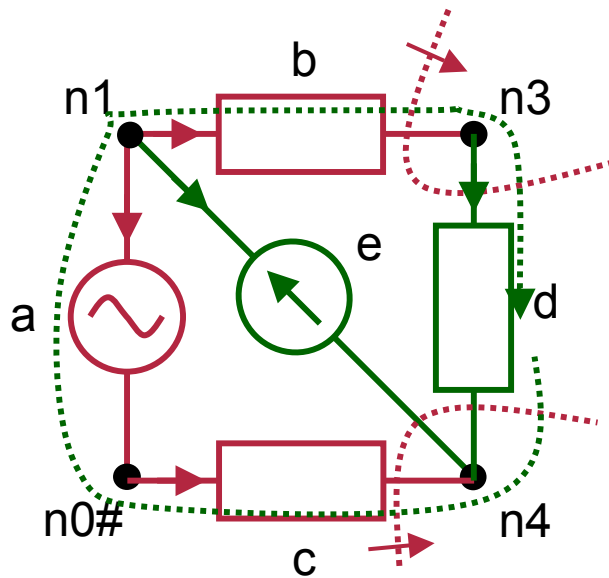

intuitive approach:

1. write the Kirchhoff current law for each fundamental cutset associated with a free twig
2. write the Kirchhoff voltage law for each fundamental loop associated with a free link


$$\left[\begin{array}{cc|c} 1 & 0 & -1 \\ 0 & 0.333 & 1 \\ \hline -1 & 1 & -4 \end{array} \right] \begin{bmatrix} v_b \\ v_c \\ i_d \end{bmatrix} = \begin{bmatrix} 0 \\ -2 \\ -10 \end{bmatrix}$$

$$\begin{bmatrix} Y_{\text{two}} & D_{\text{two},\text{lno}} \\ -B_{\text{lno},\text{two}} & -Z_{\text{lno}} \end{bmatrix} \begin{bmatrix} v_{\text{two}} \\ i_{\text{lno}} \end{bmatrix} = \begin{bmatrix} -D_{\text{two},\text{lno}} i_{\text{lno}} \\ B_{\text{lno},\text{two}} v_{\text{two}} \end{bmatrix}$$

remark: symmetric because $B_{\text{lno},\text{two}} = -D_{\text{two},\text{lno}}^T$

Circuit description (7)

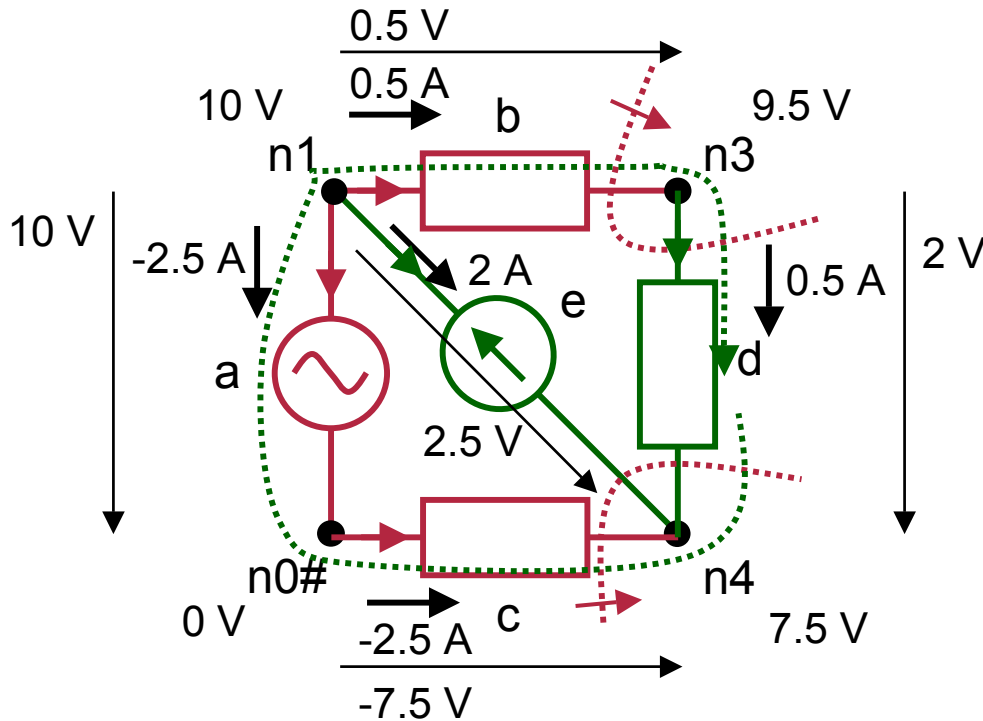7. Solve system of equations & propagate the circuit solution



solution

$$\begin{bmatrix} v_b \\ v_c \\ i_d \end{bmatrix} = \begin{bmatrix} 0.5 \\ -7.5 \\ 0.5 \end{bmatrix}$$

twig currents:

$$i_{\text{two}} = -D_{\text{two},\text{lno}} i_{\text{lno}} - D_{\text{two},\text{lni}} i_{\text{lni}}$$


$$i_{\text{twv}} = -D_{\text{twv},\text{lno}} i_{\text{lno}} - D_{\text{twv},\text{lni}} i_{\text{lni}}$$

link voltages

$$v_{\text{lno}} = -B_{\text{lno},\text{two}} v_{\text{two}} - B_{\text{lno},\text{twv}} v_{\text{twv}}$$

$$v_{\text{lni}} = -B_{\text{lni},\text{two}} v_{\text{two}} - B_{\text{lni},\text{twv}} v_{\text{twv}}$$

Particularities

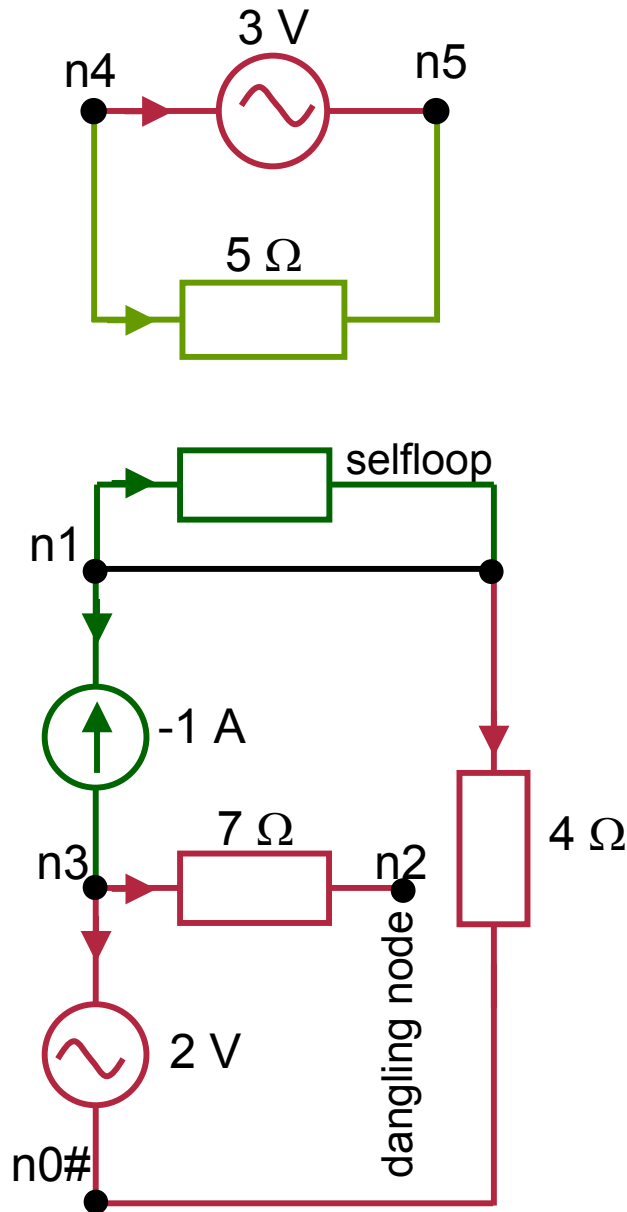

1. *Distinct circuit parts*

2. *Dangling nodes*


a branch to a dangling node
always a **twig**
associated **fundamental cutset**
only contains the twig

3. *Self-loops*

a self-loop
is always a **link**
the associated **fundamental loop**
only contains the link

Consistency check (1)

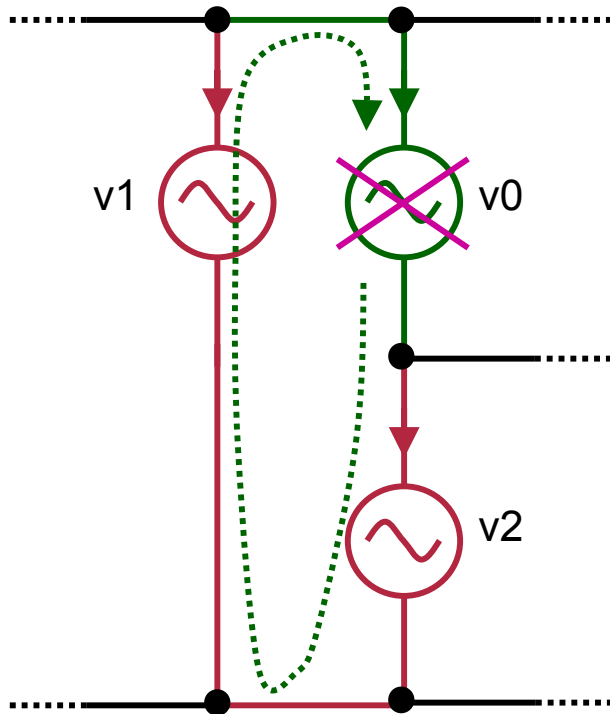1. Fundamental loop consisting of voltage sources



Problem: a voltage source is necessarily selected as **link**

Treatment: check the Kirchhoff voltage law in the associated **fundamental loop**

e.g. $v_0 - v_1 + v_2 = 0$??

if valid


omit the voltage source link

if not valid

the circuit has no solution

Consistency check (2)

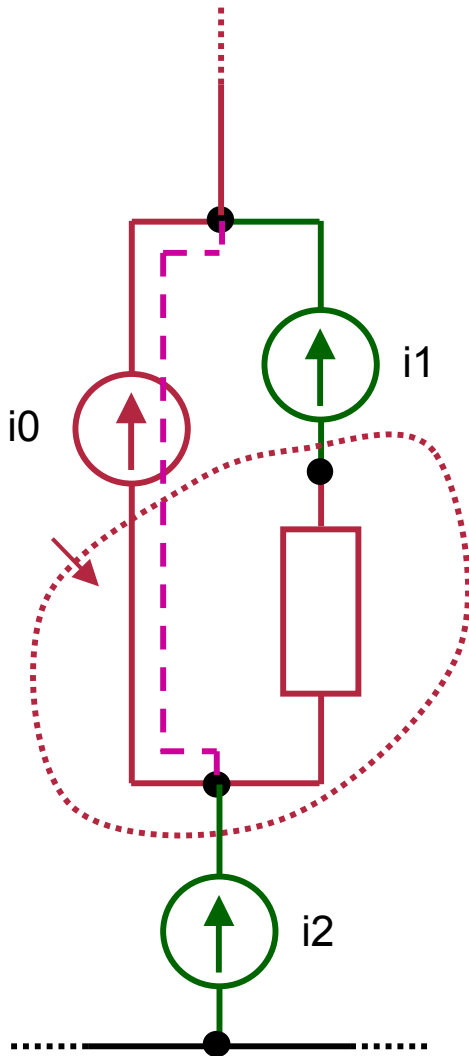2. Fundamental cutset consisting of current sources



Problem: a current source is necessarily selected as **twig**

Treatment: check the Kirchhoff current law in the associated **fundamental cutset**

$$\text{e.g. } i_0 + i_1 - i_2 = 0 ??$$

if valid


replace the current source twig by a short-circuit connection

if not valid

the circuit has no solution

Partial transformation (1)

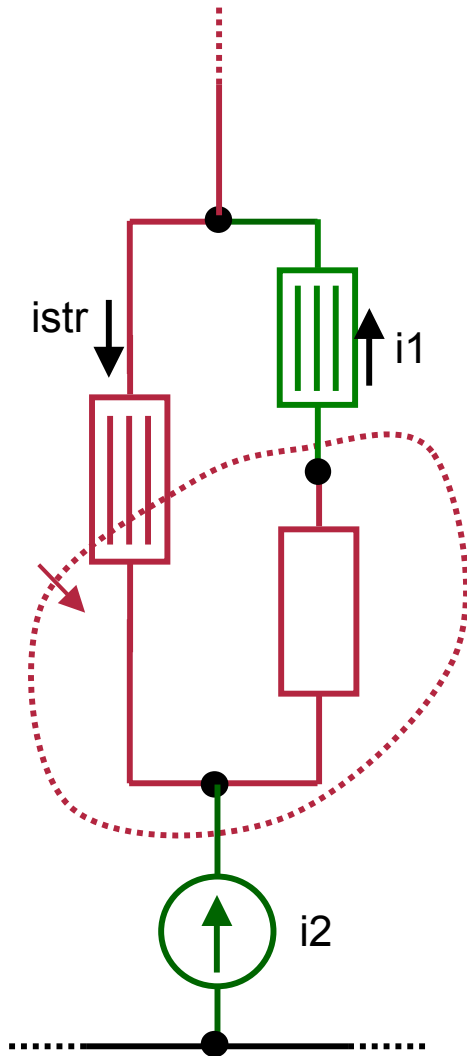1. Stranded conductor being selected as twig



Problem: a **stranded conductor** (current-driven branch) is necessarily selected as **twig**


Property: $\text{priority}(\text{twig}) \geq \text{priority}(\text{branch})$,
 $\forall \text{branch} \in \text{associated fundamental cutset}$

Treatment: apply the Kirchhoff current law in the associated **fundamental cutset** to express the stranded-conductor current in terms of link currents
 e.g. $i_{\text{str}} = i_1 + i_2$

~ small and independent Schur complements

Partial transformation (2)

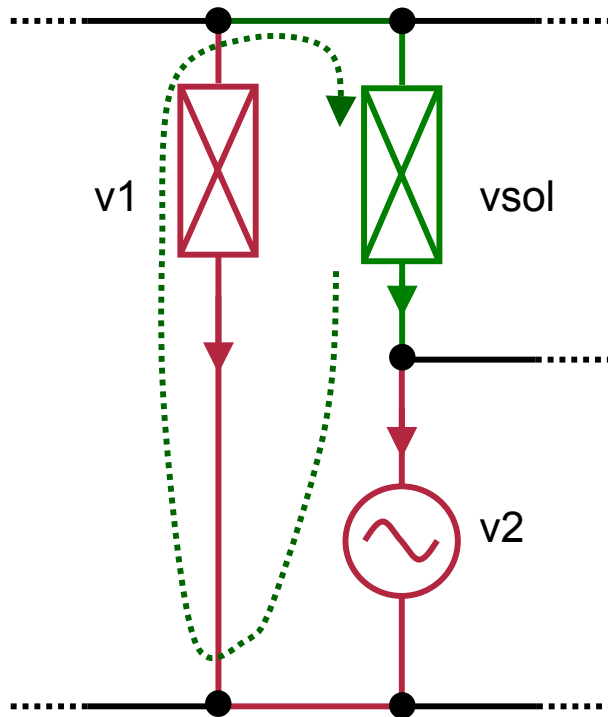2. Solid conductor being selected as link



Problem: a **solid conductor** (voltage-driven branch) is necessarily selected as **link**


Property: $\text{priority}(\text{link}) \leq \text{priority}(\text{branch})$,
 $\forall \text{branch} \in \text{associated fundamental loop}$

Treatment: apply the Kirchhoff voltage law in the associated **fundamental loop** to express the solid-conductor voltage in terms of twig voltage
 e.g. $v_{\text{sol}} = v_1 + v_2$

~ small and independent Schur complements

Topological changes (1)

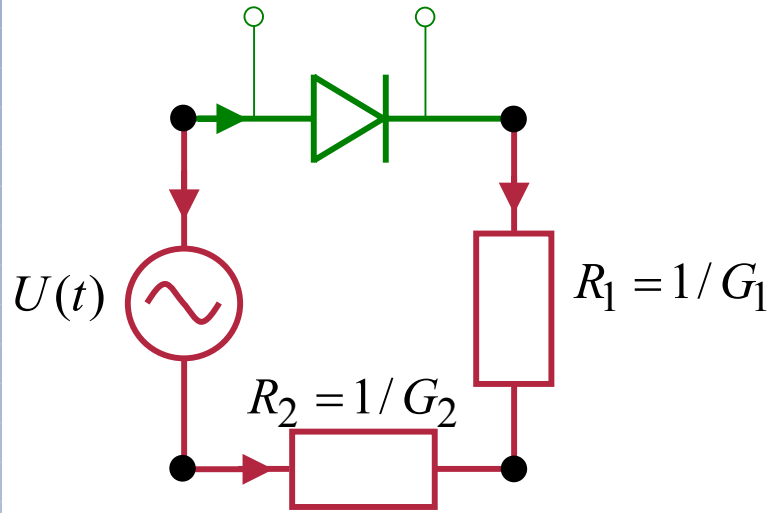
1. Switching elements closes (switch, diode, thyristor,...)



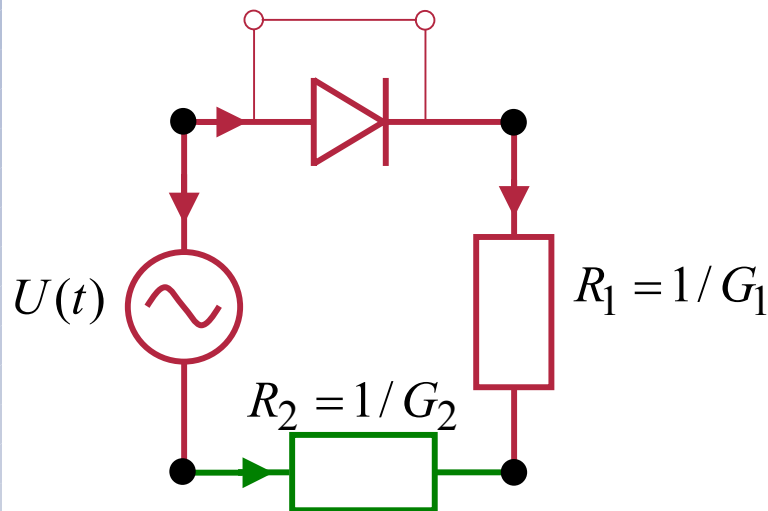Problem: the priority of a branch increases during (transient) simulation

$$\begin{bmatrix} G_1 & 0 \\ 0 & G_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$


Treatment: consider associated fundamental loop and possibly change link/twig-mode with the branch with the lowest priority



$$\begin{bmatrix} G_1 & 1 \\ 1 & -R_2 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ U \end{bmatrix}$$


Topological changes (2)

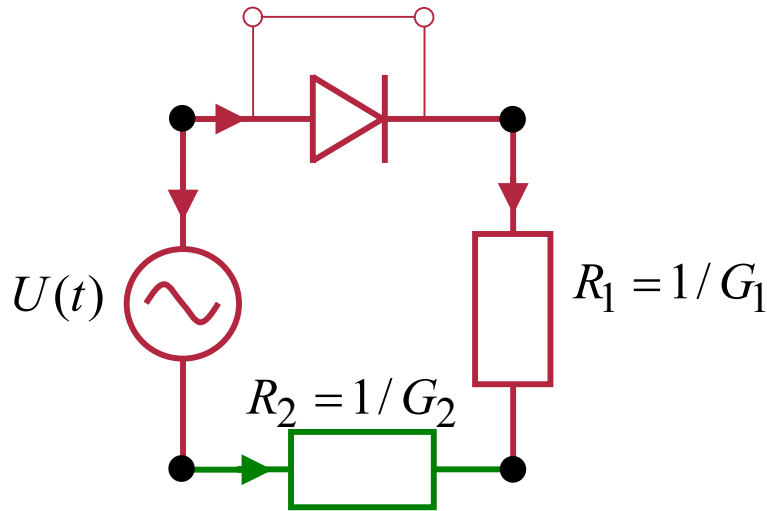1. Switching element opens (switch, diode, thyristor,...)



$$\begin{bmatrix} G_1 & 1 \\ 1 & -R_2 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ U \end{bmatrix}$$

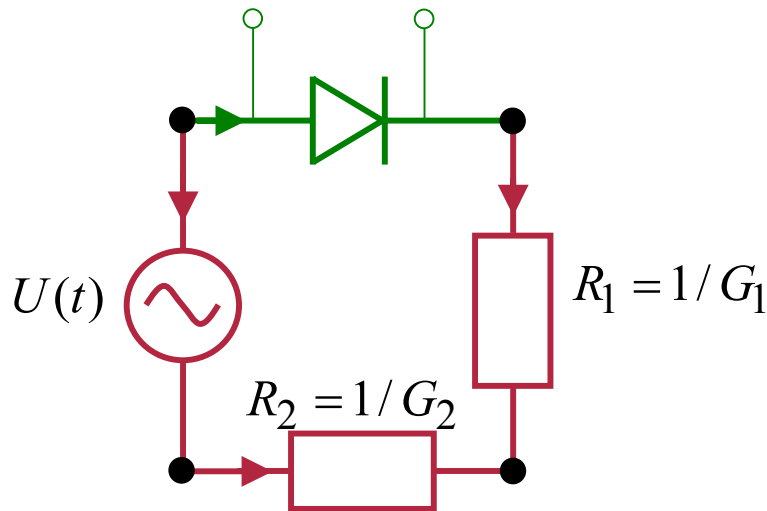Treatment: consider associated fundamental cutset and possibly change link/twig-mode with the branch with the highest priority



$$\begin{bmatrix} G_1 & 0 \\ 0 & G_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Field-circuit coupling (3)

KCL applied to the fundamental cutsets

$$i_t + Di_l = 0$$

KVL applied to the fundamental loops

$$v_l + Bv_t = 0$$

magnetodynamic PDE
reluctivity magnetic vector potential
conductivity

$$\nabla \times (\nu \nabla \times \mathbf{A}) + j\omega\sigma\mathbf{A} = -\sigma \nabla V$$



FE equations:

cutset equations:

loop equations:

$$\begin{bmatrix} k_{ij} + j\omega l_{ij} & q_{it} & -p_{il} \\ q_{sj} & \chi G_m & \chi D \\ -p_{kj} & -\chi B & -\chi R_m \end{bmatrix} \begin{bmatrix} A_{zj} \\ v_t \\ i_l \end{bmatrix} = \begin{bmatrix} 0 \\ \chi I_{app} \\ -\chi V_{app} \end{bmatrix}$$

$$i_t = G_m v_t - j\omega q_{mj} A_{zj}$$


twig branch relations

symmetrisation factor χ
& $B = -D^T$

symmetric !

$$v_l = R_m i_l + j\omega p_{mj} A_{zj}$$

link branch relations

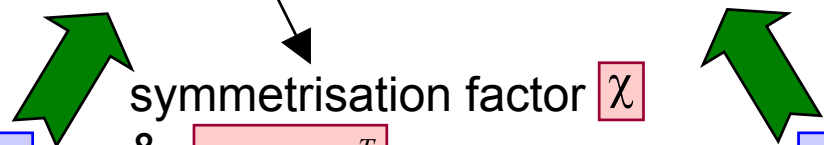

Algebraic solution (1)

Coupled system matrix

- symmetric/indefinite

FE/FIT part

- sparse (no fill-in)
- changes due to non-linearities

Circuit part

- dense
- changes due to non-linearities & switching

Coupling blocks


- dense
- does not change

#positive-eigenvalues

= #FE/FIT-dofs + #cutset-equations

#negative-eigenvalues

= #loop-equations

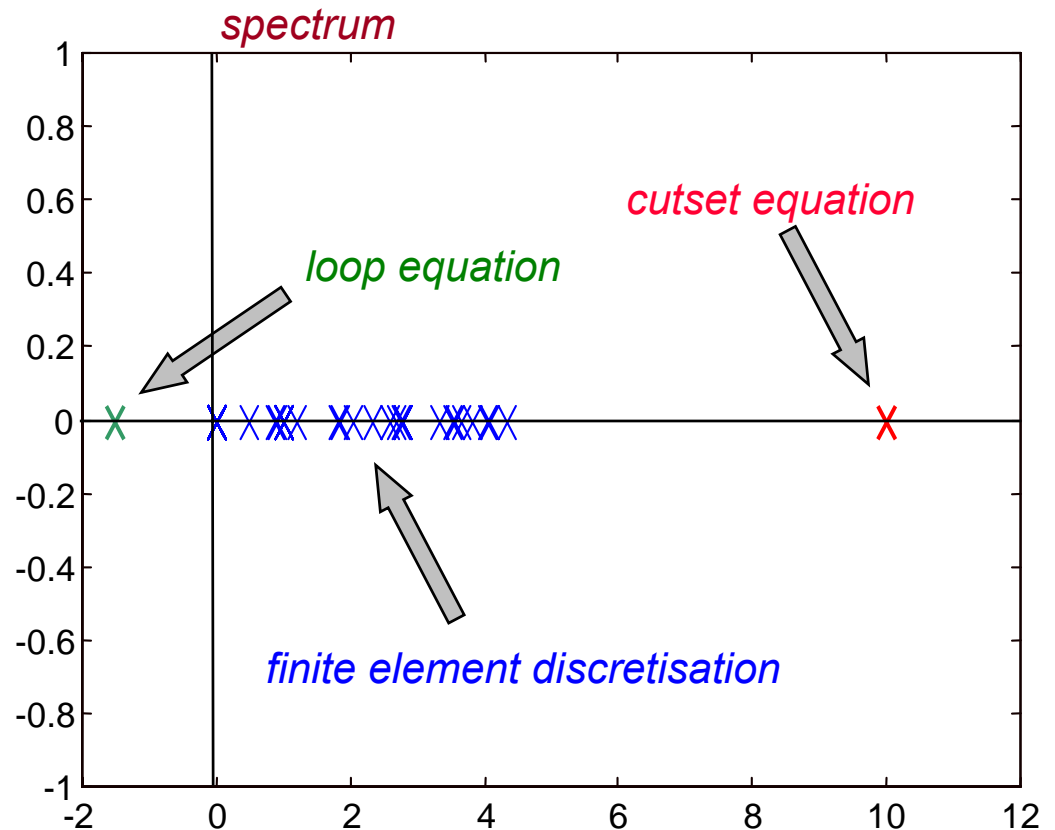

Algebraic solution (2)

	solver	preconditioner
$\begin{bmatrix} K & B^T \\ B & C \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} f \\ g \end{bmatrix}$	MINRES QMR MINRES/QMR	SSOR SSOR BJac (AMG,LU)
Schur complement 1 $(K - B^T C^{-1} B)x = f - B^T C^{-1} g$	CG(LU)	? SSOR/AMG ? DD
Schur complement 2 $(C - BK^{-1} B^T)y = g - BK^{-1} f$	LU(AMGCG)	? LU ? DD

Algebraic solution (3)

Algebraic multigrid for field-circuit coupled systems
(Dr. Domenico Lahaye, CRS4, Cagliari, Italy)

fine grid system:

$$\begin{bmatrix} K & B^T \\ B & C \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} f \\ g \end{bmatrix}$$



prolongation: $P_{H \rightarrow h}$
restriction: $R_{h \rightarrow H} = P_{H \rightarrow h}^T$

coarse grid system:


$$\begin{bmatrix} P_{H \rightarrow h}^T & \\ & I \end{bmatrix} \begin{bmatrix} K_H & B_H^T \\ B_H & C \end{bmatrix} \begin{bmatrix} P_{H \rightarrow h} & \\ & I \end{bmatrix} \begin{bmatrix} x_H \\ y_H \end{bmatrix} = \begin{bmatrix} P_{H \rightarrow h}^T & \\ & I \end{bmatrix} \begin{bmatrix} f \\ g \end{bmatrix}$$

smoother: block-Jacobi with

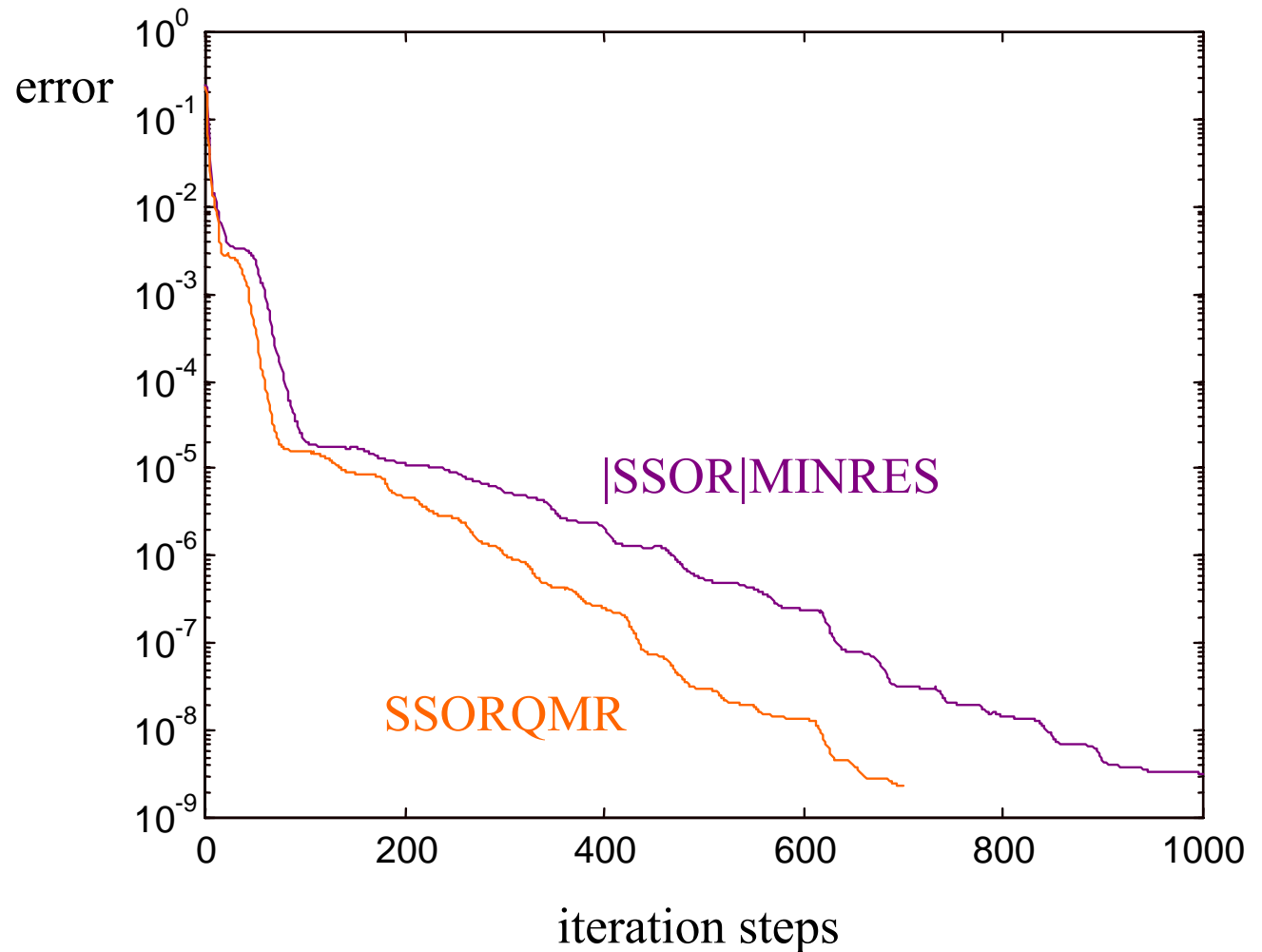1. Gauss-Seidel for the FE/FIT unknowns
2. no smoothing or an exact solution for the circuit unknowns


Algebraic solution (4)

Performance of an indefinite and definite preconditioner



Algebraic solution (5)

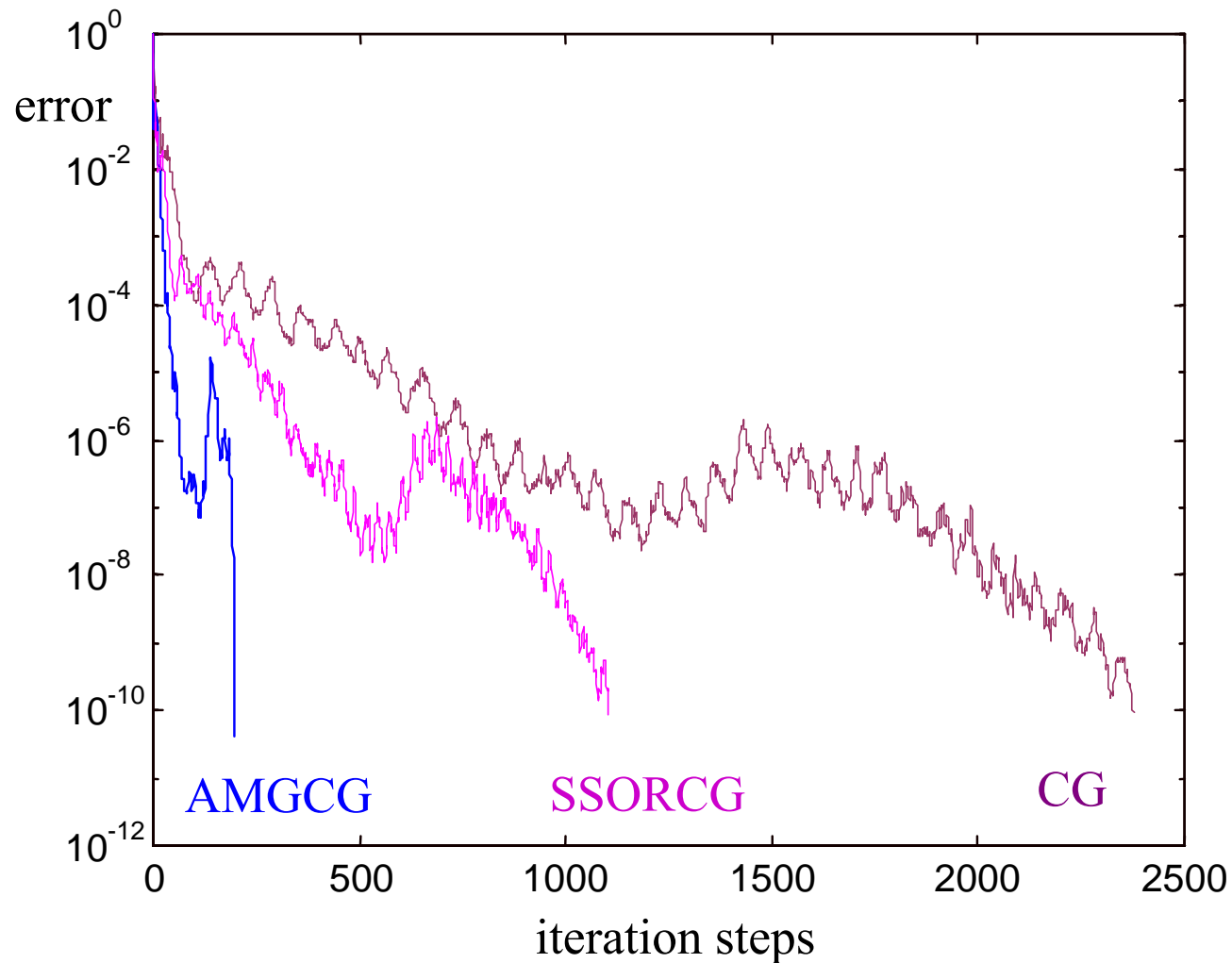Preconditioning of the Schur-complement system



Algebraic solution (6)

Iteration counts and computation times of the iterative system solution for 1 time step of a transient simulation.

	iteration steps	computation time (s)
MINRES	1997	59.80
QMR	1330	40.23
GMRES	1031	159.71
SSOR MINRES	476	11.03
SSORQMR	320	7.41
SSORGMRES	312	38.13
JAC(SSOR,LU)GMRES	325	53.91
JAC(AMG,LU)QMR	245	5.23
CG*	2376	30.06
SSORCG*	1105	17.32
AMGCG*	199	9.28

without preconditioning

non-symmetric ↔ symmetric solver

block preconditioning


Schur complement

indefinite ↔ definite preconditioning

& Domenico Lahaye: Algebraic multigrid for field-circuit coupled systems

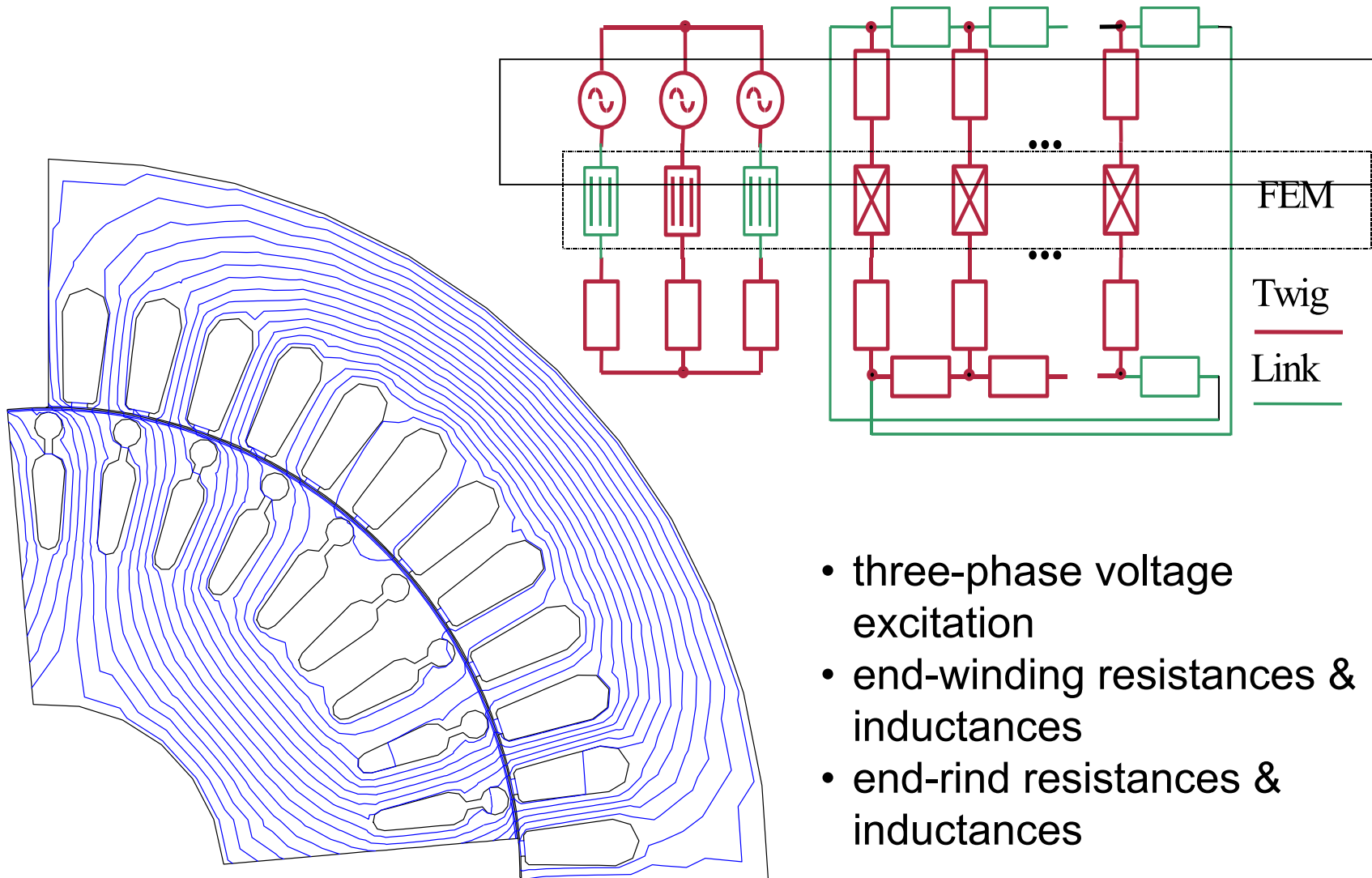Examples (1)

Time-harmonic simulation of a three-phase induction machine







- three-phase voltage excitation
- end-winding resistances & inductances
- end-ring resistances & inductances

Examples (2)




1. magnetic field + magnetic circuit

2. magnetic field + analytical model + electric circuit

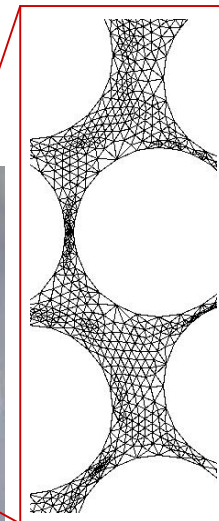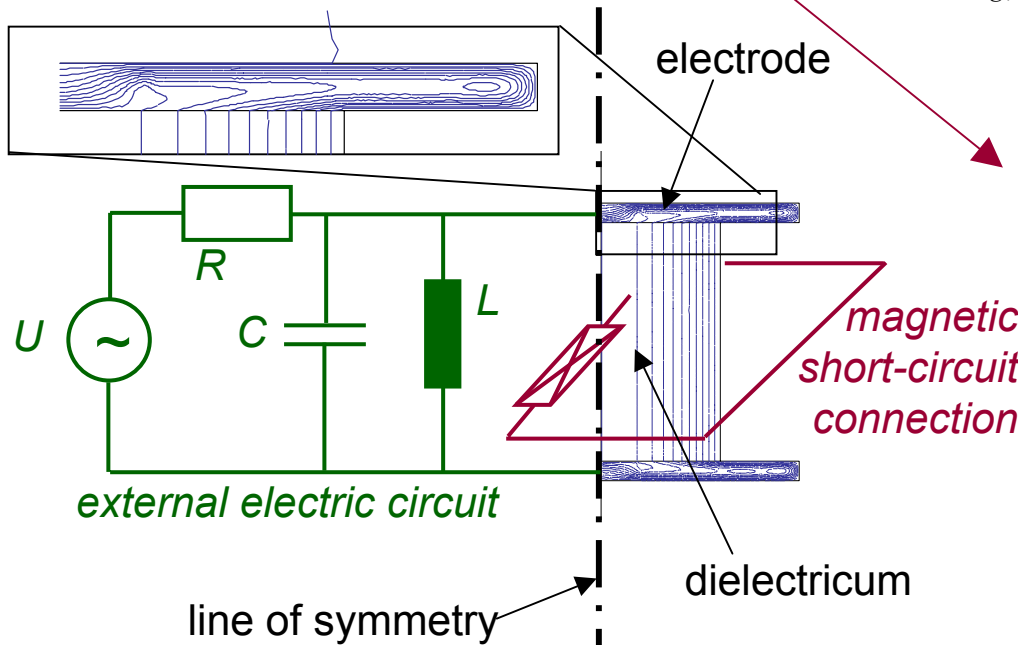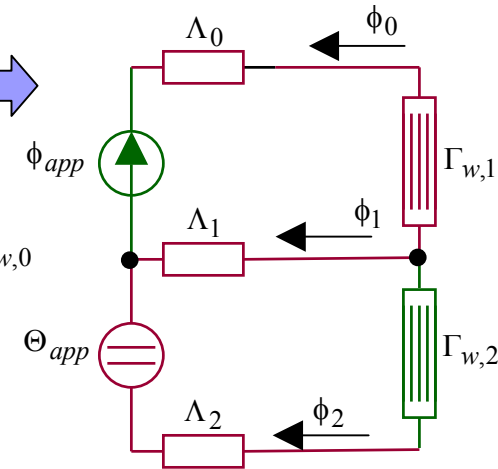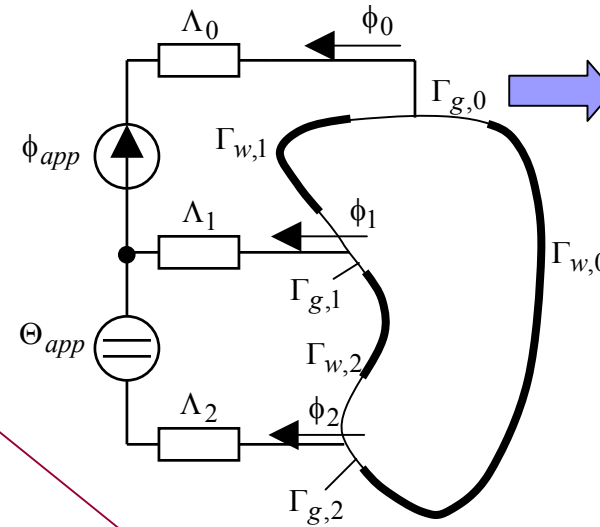3. electrokinetic field + magnetic circuit + electric circuit







More general conductor systems ?

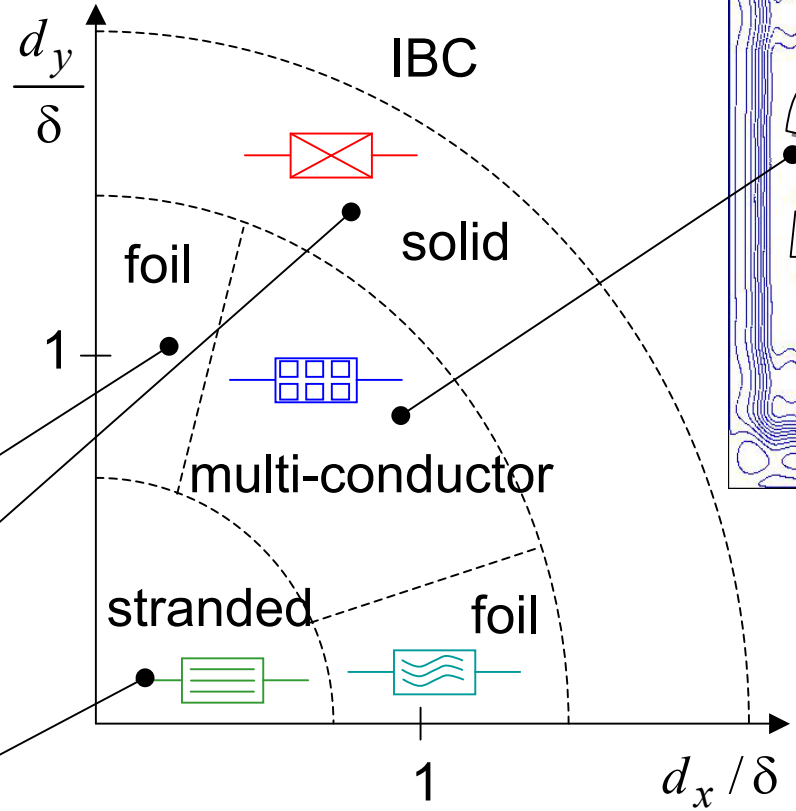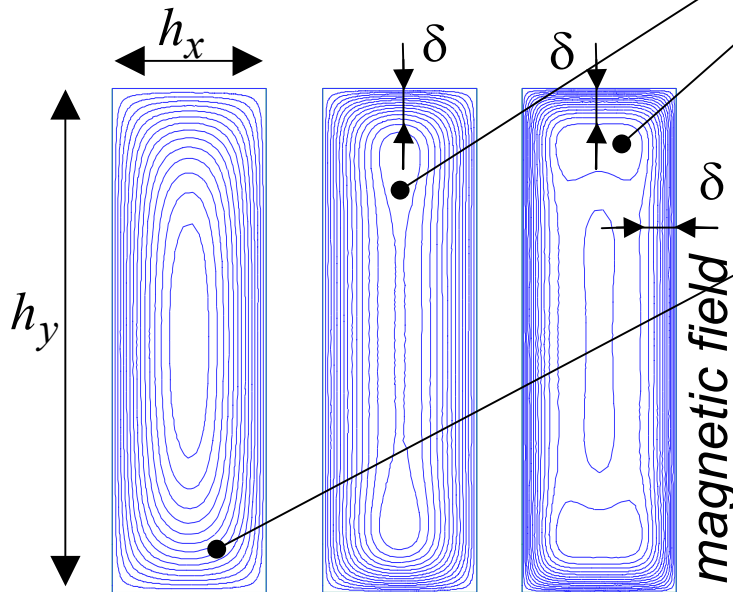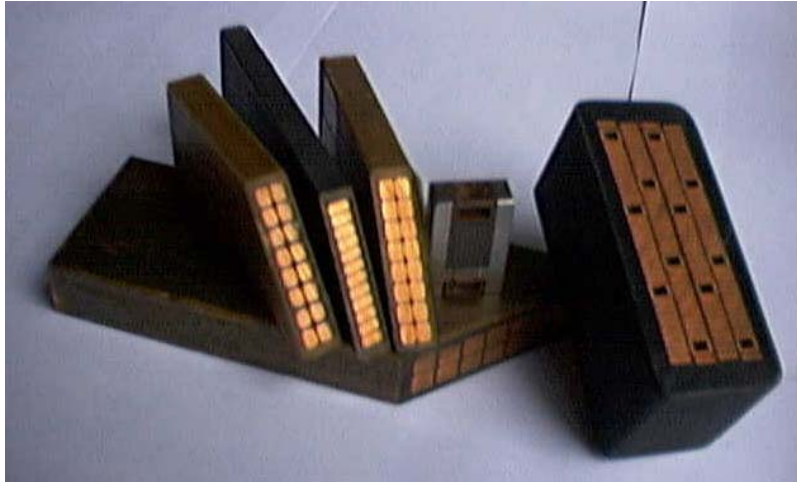


$$\delta = \sqrt{\frac{1}{\pi f \sigma \mu}} \quad \text{skin depth}$$

Foil windings






foil winding transformer

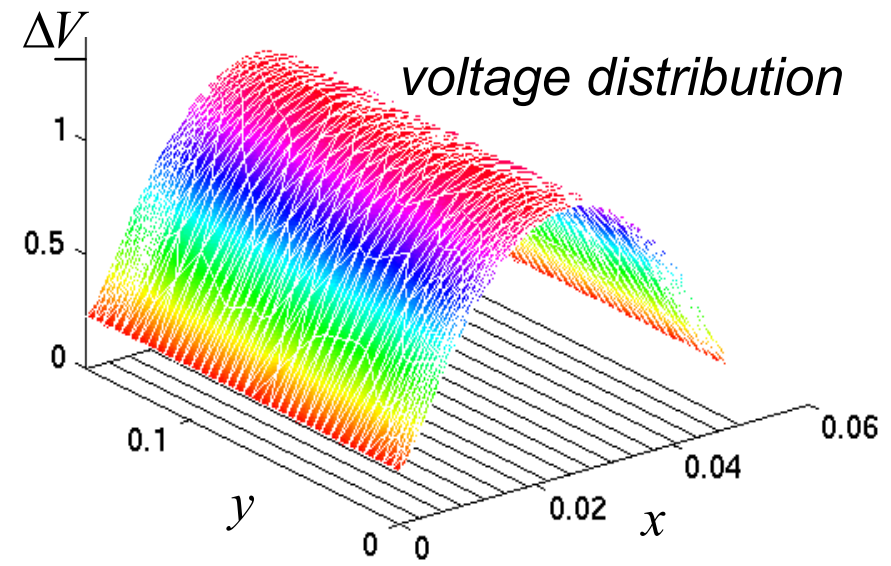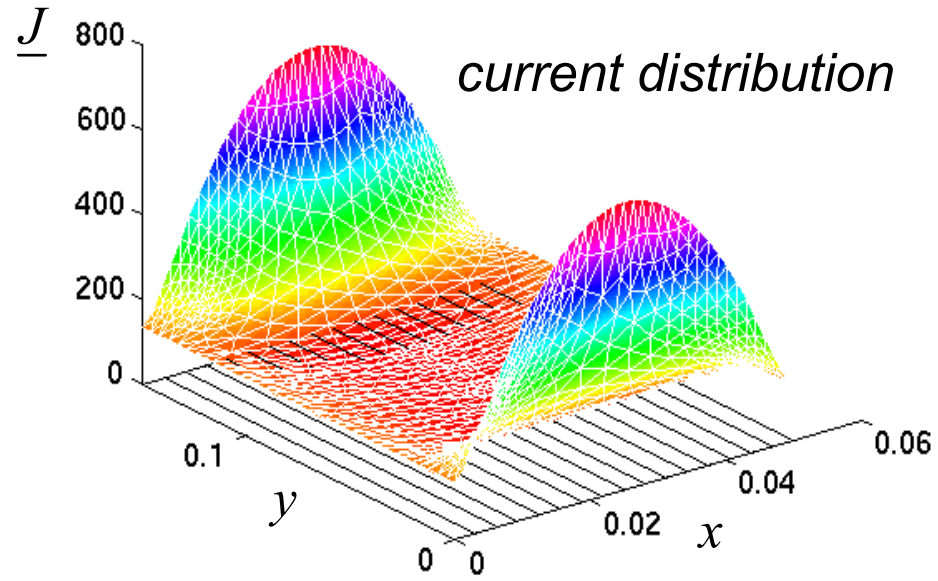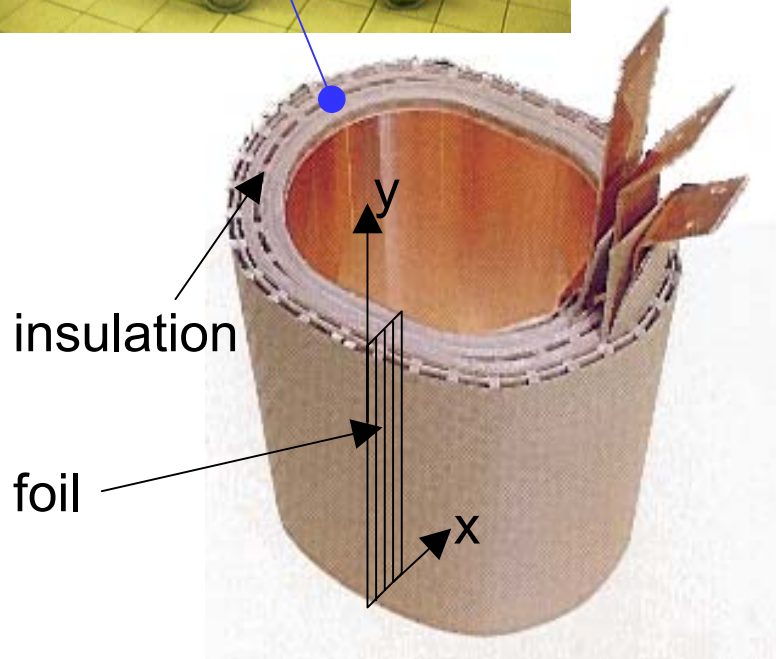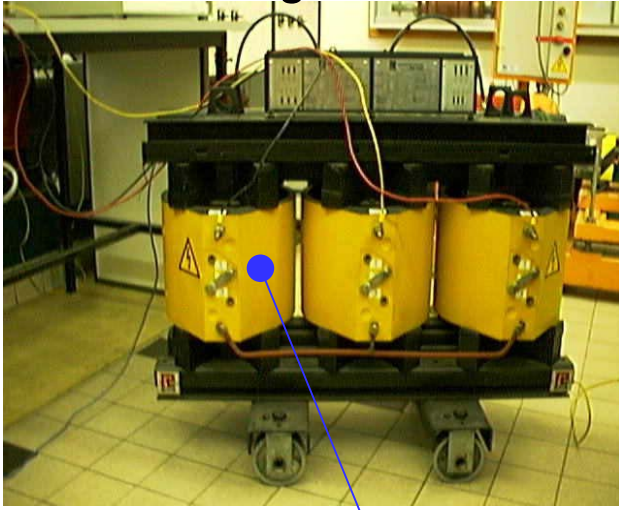

Foil conductor model

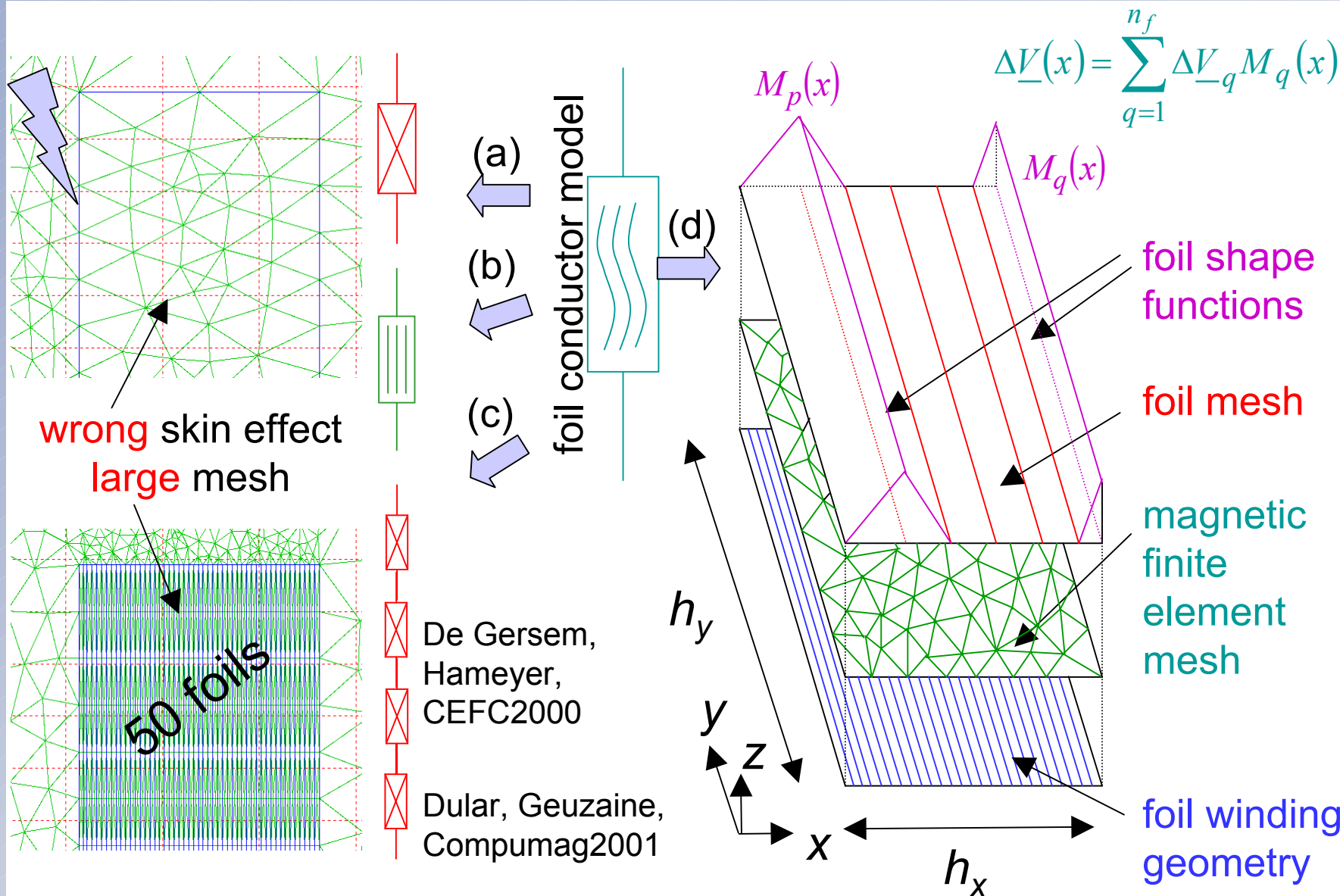

Foil winding transformer

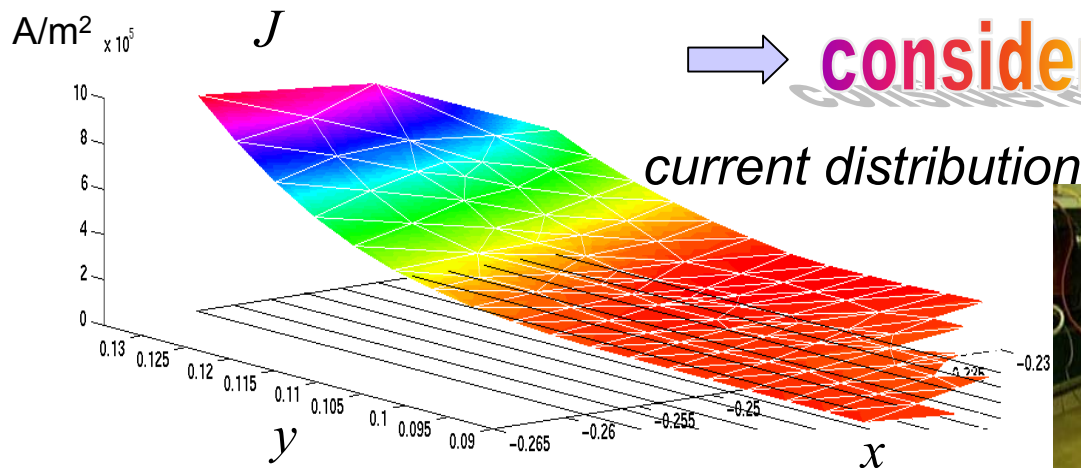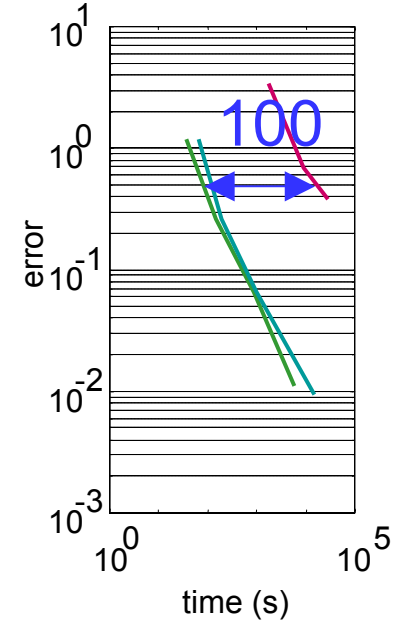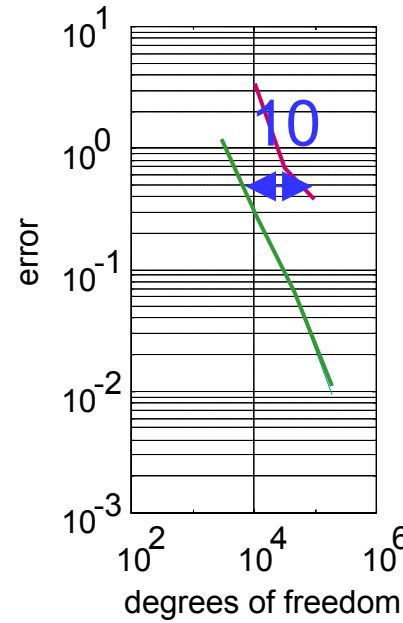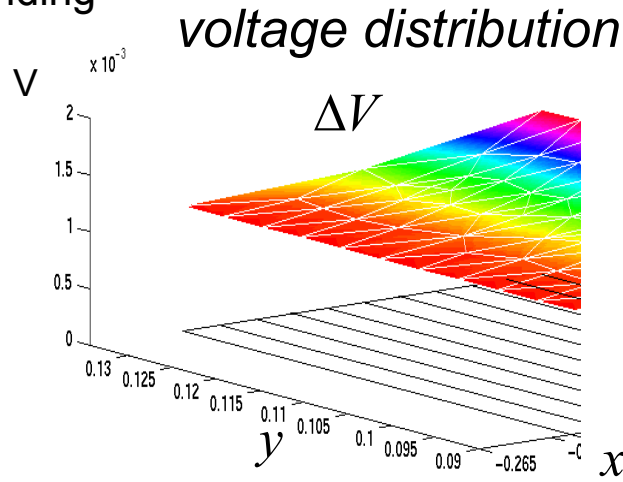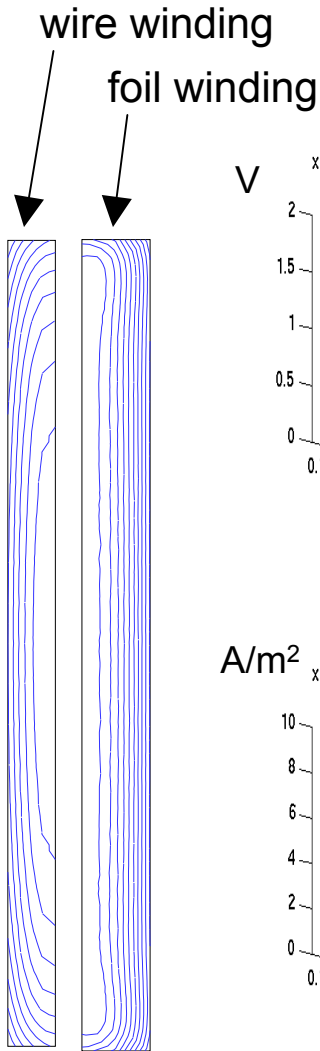


→ considerable saving




Superconductive magnets (1)



fast ramped magnets

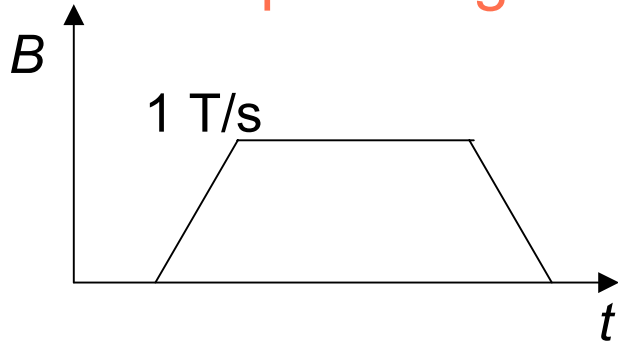

yoke: eddy currents & hysteresis
 superconductive filaments: persistent & coupling currents
 Rutherford cable: cable eddy currents/magnetisation

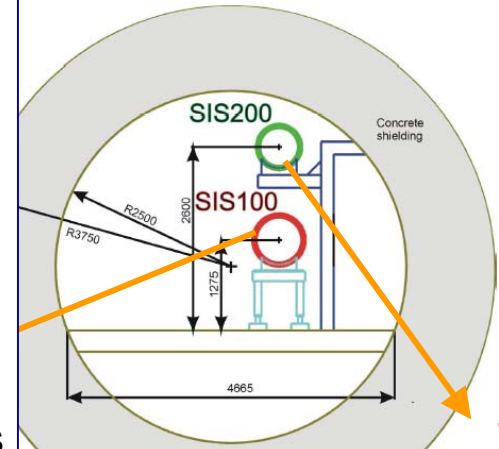


SIS300

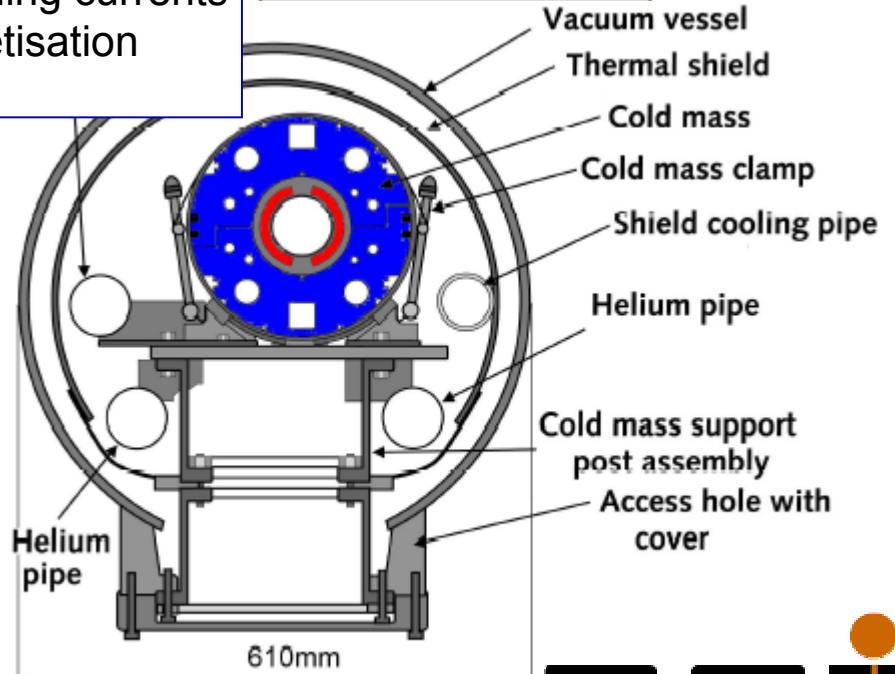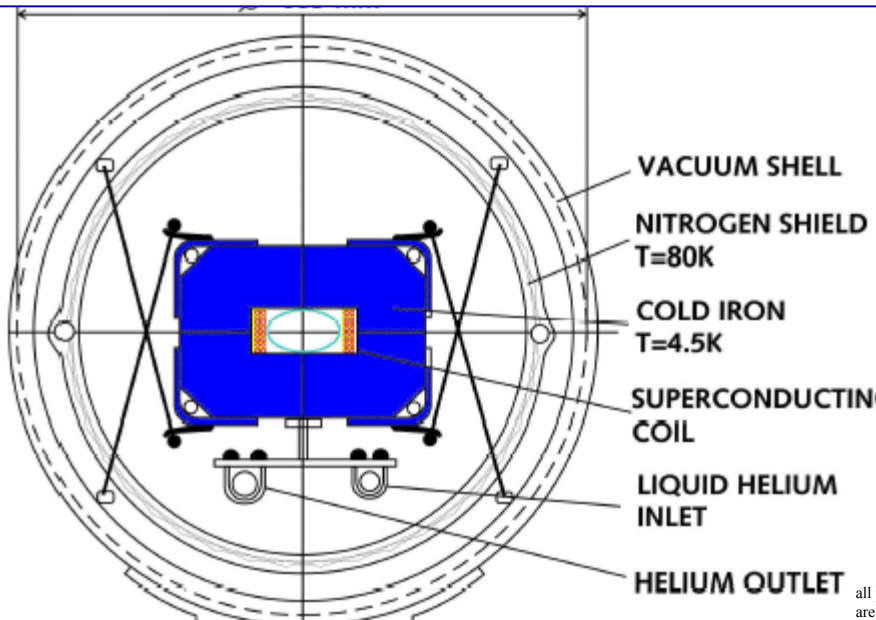


all photographs and figures of accelerator facilities in the rest of this presentation are copyright of the Gesellschaft für Schwerionenforschung, Darmstadt


Superconductive magnets (2)

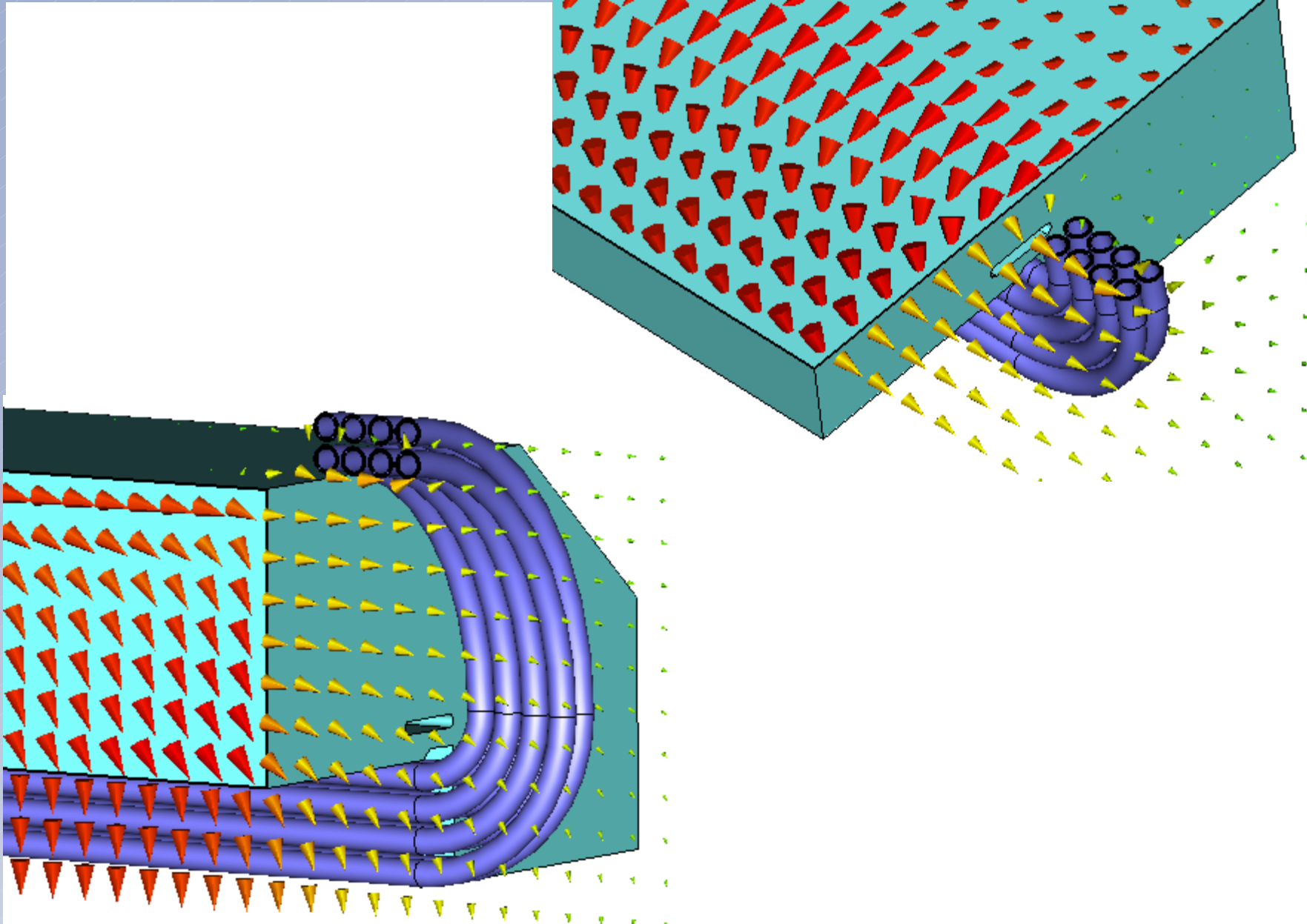


Rutherford Cable (1)

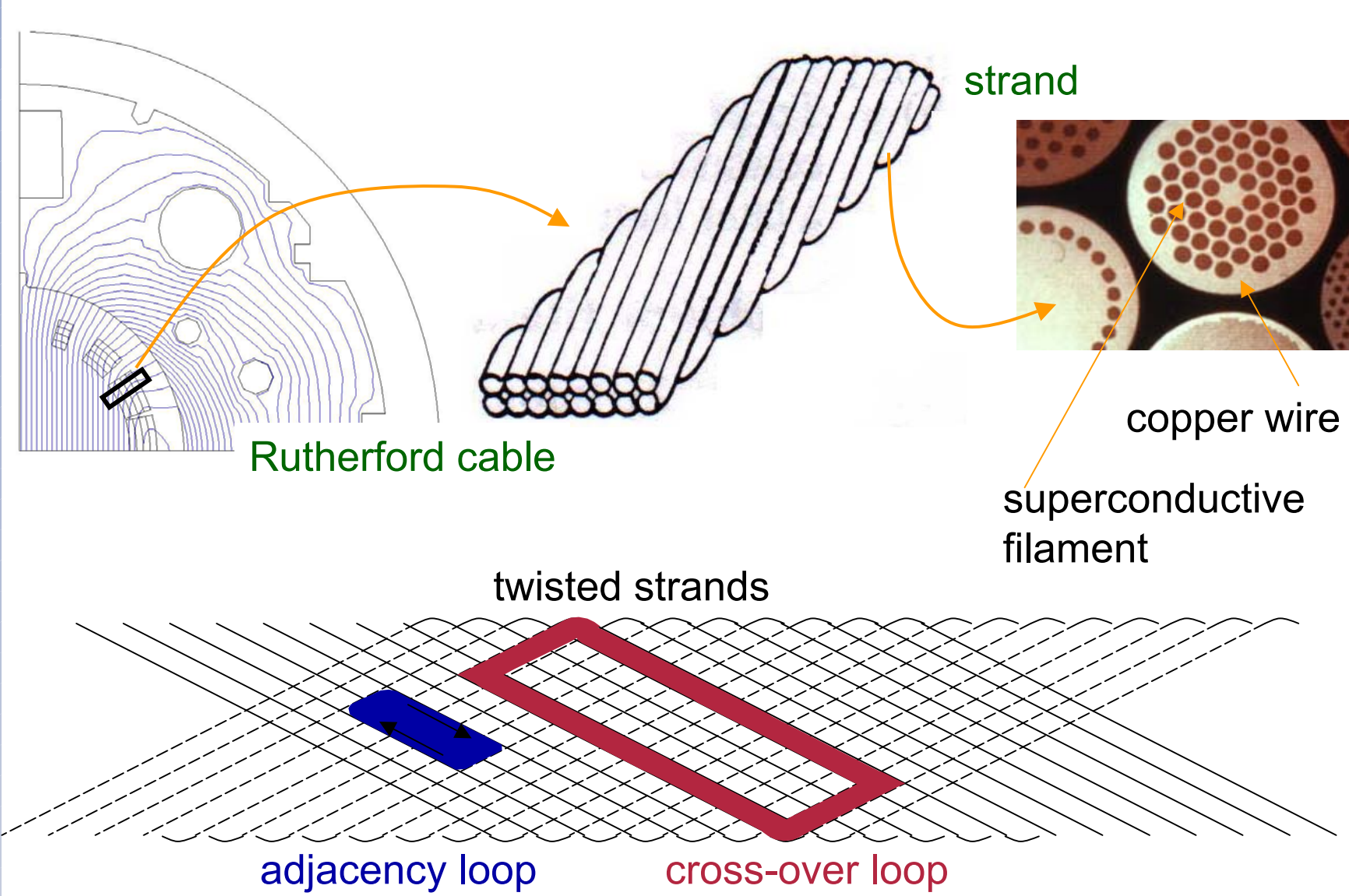


Rutherford Cable (2)

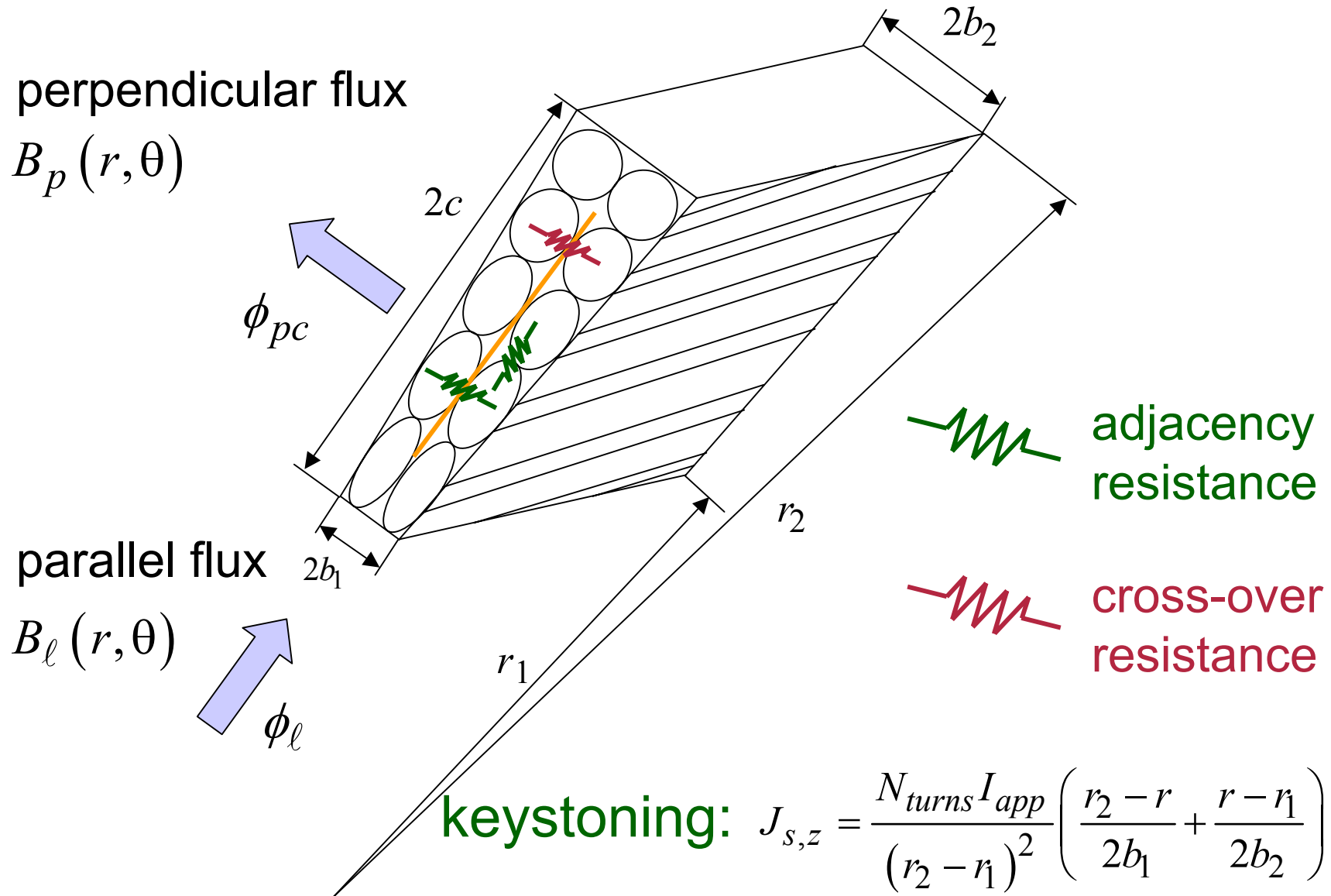

Magnetic flux density

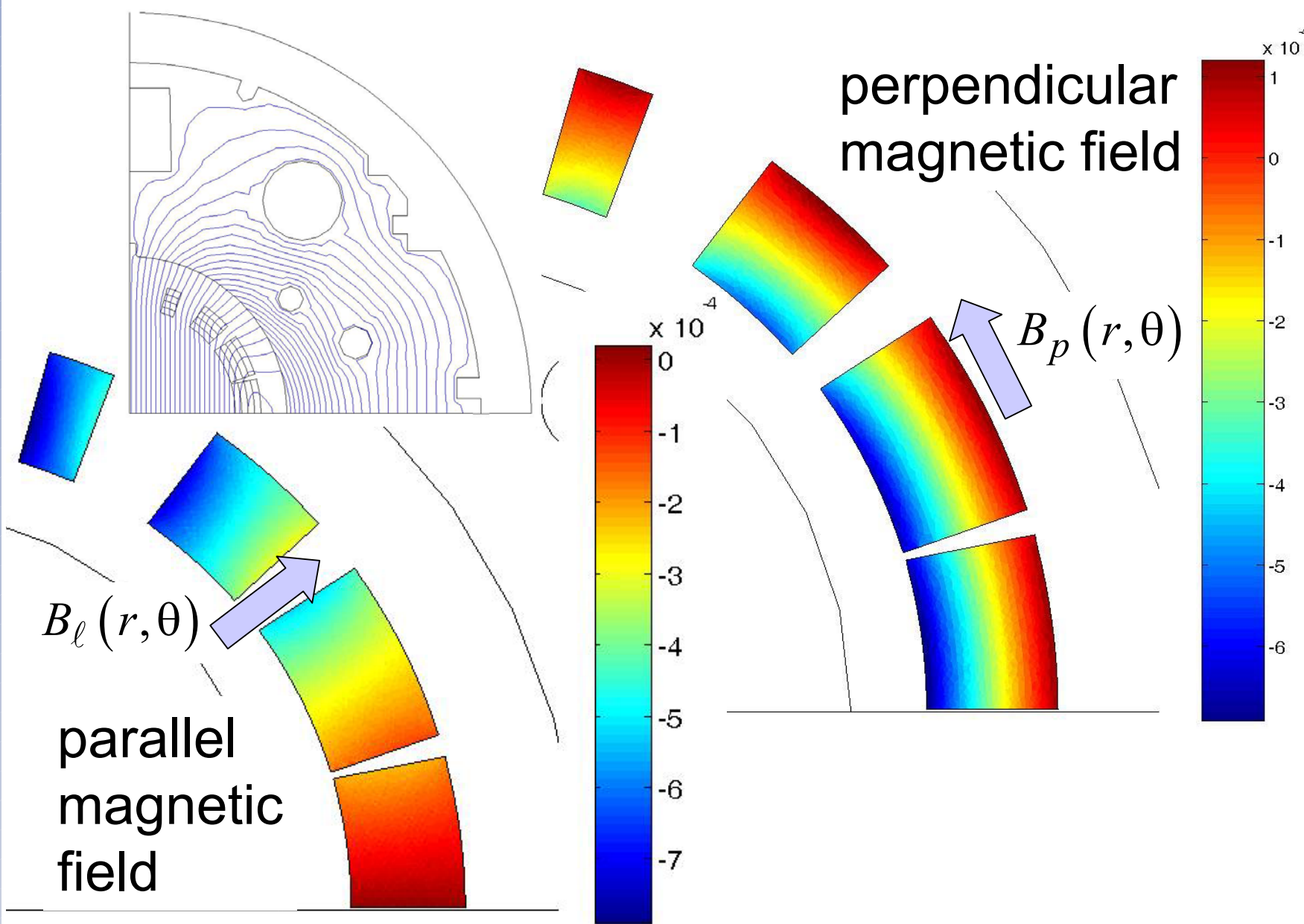

Adjacency eddy current (1)

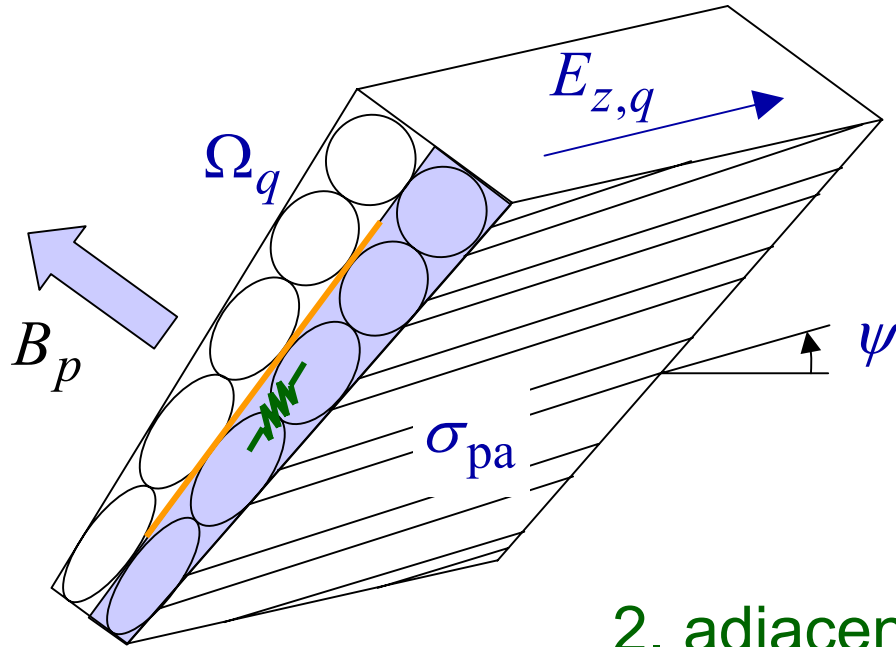

due to perpendicular magnetic field

1. additional discretisation for unknown electric field $E_{z,q}$:

$$E_z(x, y) = \sum_q E_{z,q} M_q(x, y)$$

2. adjacency eddy current density :

$$J_{pa,z}(r, \theta) = \sigma_{pa} E_{z,q} - \sigma_{pa} \frac{\partial A_z}{\partial t}$$

3. netto current through $\Omega_q = 0$

$$I_{z,q} = \int_{\Omega_q} J_{pa,z}(r, \theta) d\Omega = 0$$

additional constraint !


Adjacency eddy current (2)

additional load term for magnetic FE model

$$g_{pa} = M_{pa} \frac{\partial u}{\partial t} - Z_{pa} e_{pa}$$

additional constraint
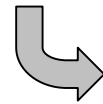
$$-Z_{pa}^T \frac{\partial u}{\partial t} + G_{pa} e_{pa} = 0$$



degrees of freedom for $E_{z,q}$


$$\begin{bmatrix} M_{pa} & 0 \\ Z_{pa}^T & 0 \end{bmatrix} \frac{\partial}{\partial t} \begin{bmatrix} u \\ e_{pa} \end{bmatrix} + \begin{bmatrix} K & Z_{pa} \\ 0 & G_{pa} \end{bmatrix} \begin{bmatrix} u \\ e_{pa} \end{bmatrix} = \begin{bmatrix} f \\ 0 \end{bmatrix}$$

$$M_{pa,ij} = \int_{\Omega} \sigma_{pa} N_i(x, y) N_j(x, y) d\Omega$$


$$Z_{pa,iq} = \int_{\Omega} \sigma_{pa} N_i(x, y) M_q(x, y) d\Omega$$

$$G_{pa,pq} = \int_{\Omega} \sigma_{pa} M_p(x, y) M_q(x, y) d\Omega$$

Adjacency eddy current (3)

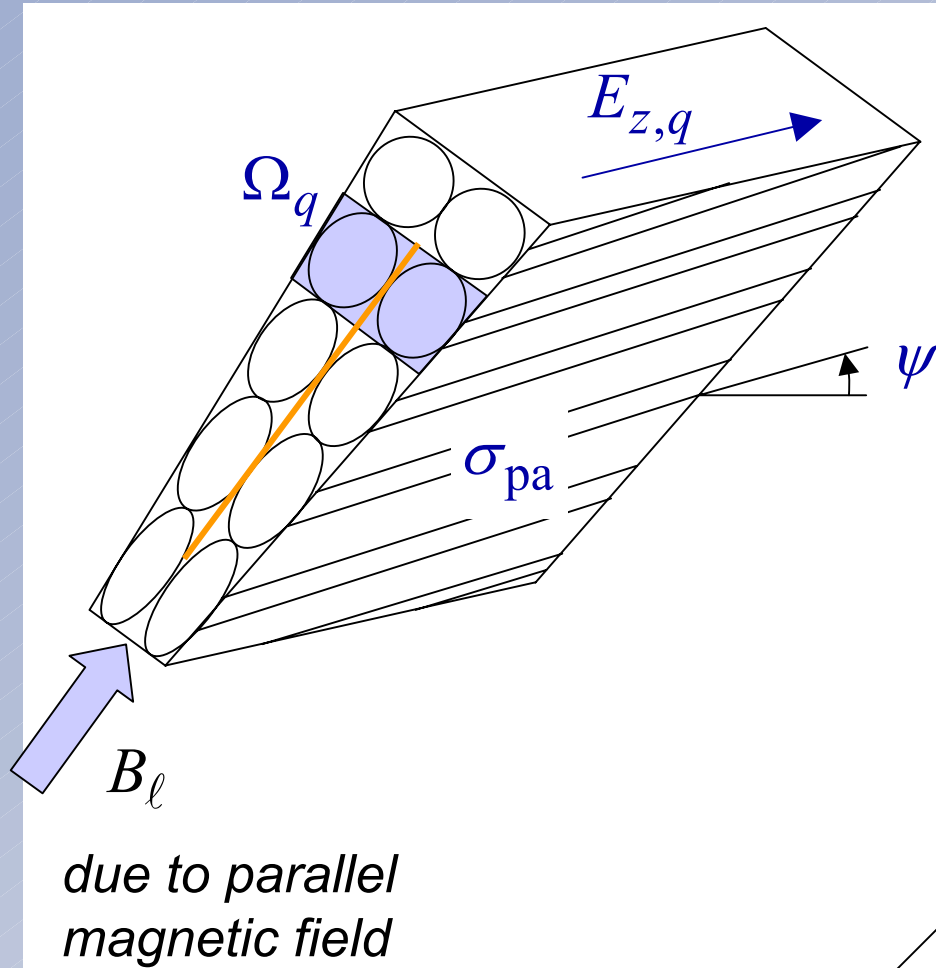


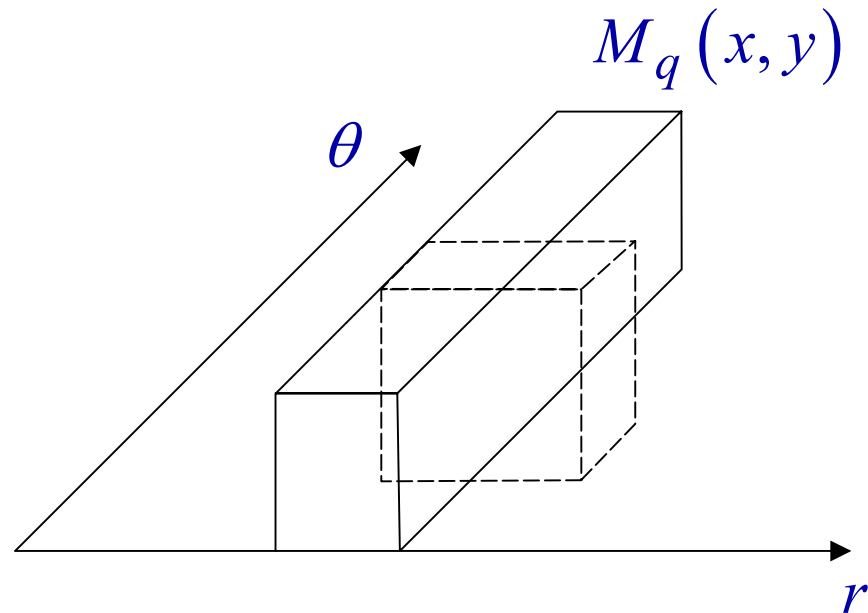shape functions $M_q(x, y)$
related (but not necessarily equal)
to the zones of current
redistribution




Adjacency eddy current

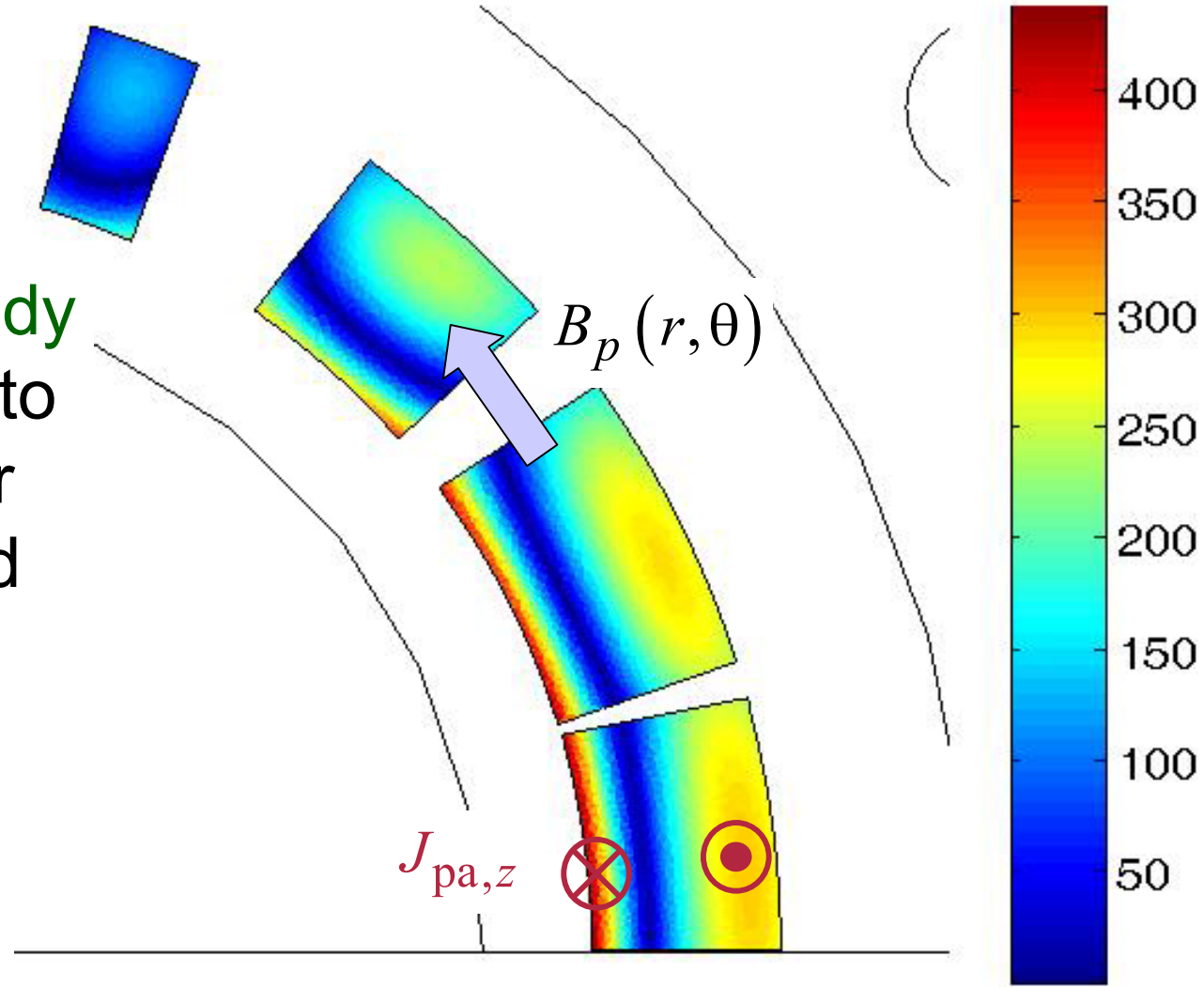adjacency eddy currents due to perpendicular magnetic field



Cross-over eddy current (1)

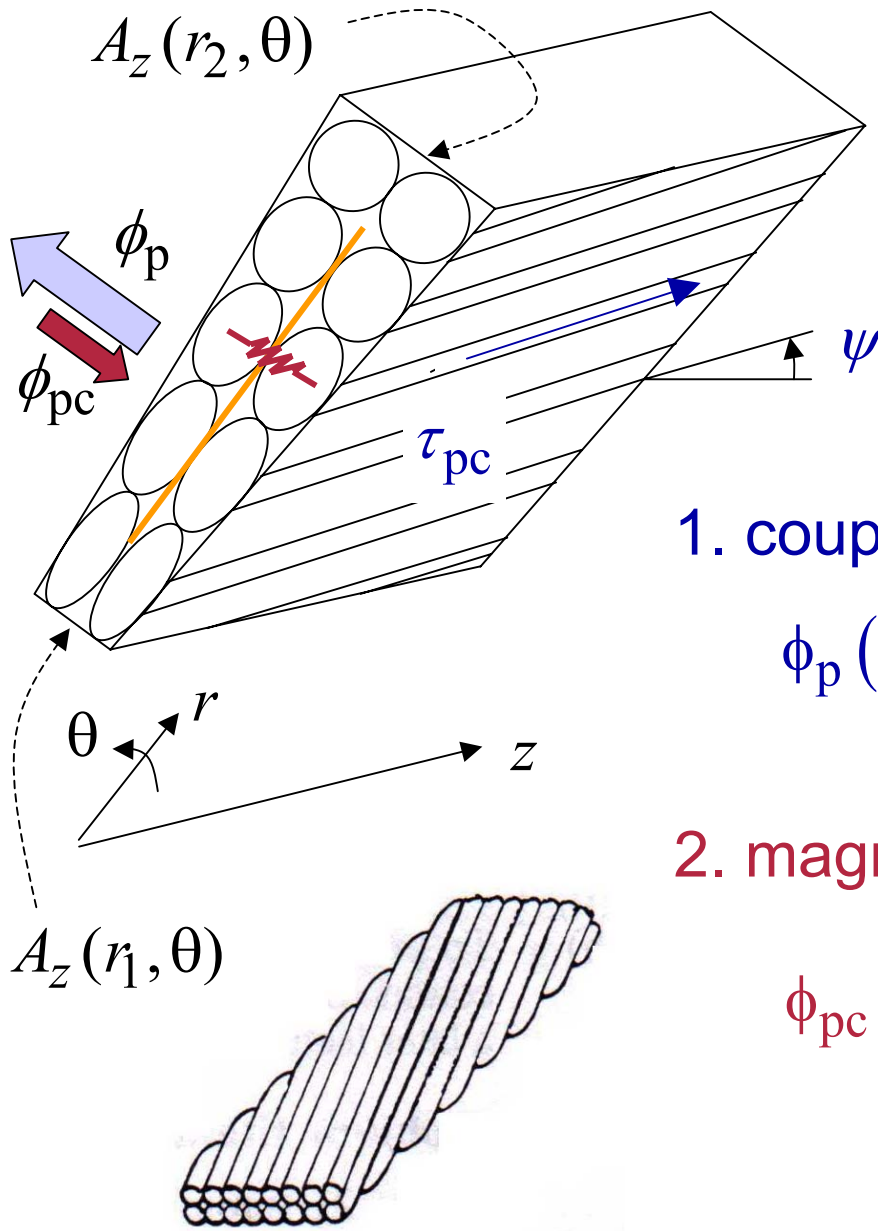

1. coupled flux


$$\phi_p(\theta) = \ell_z (A_z(r_2, \theta) - A_z(r_1, \theta))$$

2. magnetisation


$$\phi_{pc}(\theta) = \tau_{pc} \frac{\partial \phi_p(\theta)}{\partial t}$$

 *time constant*

Cross-over eddy current

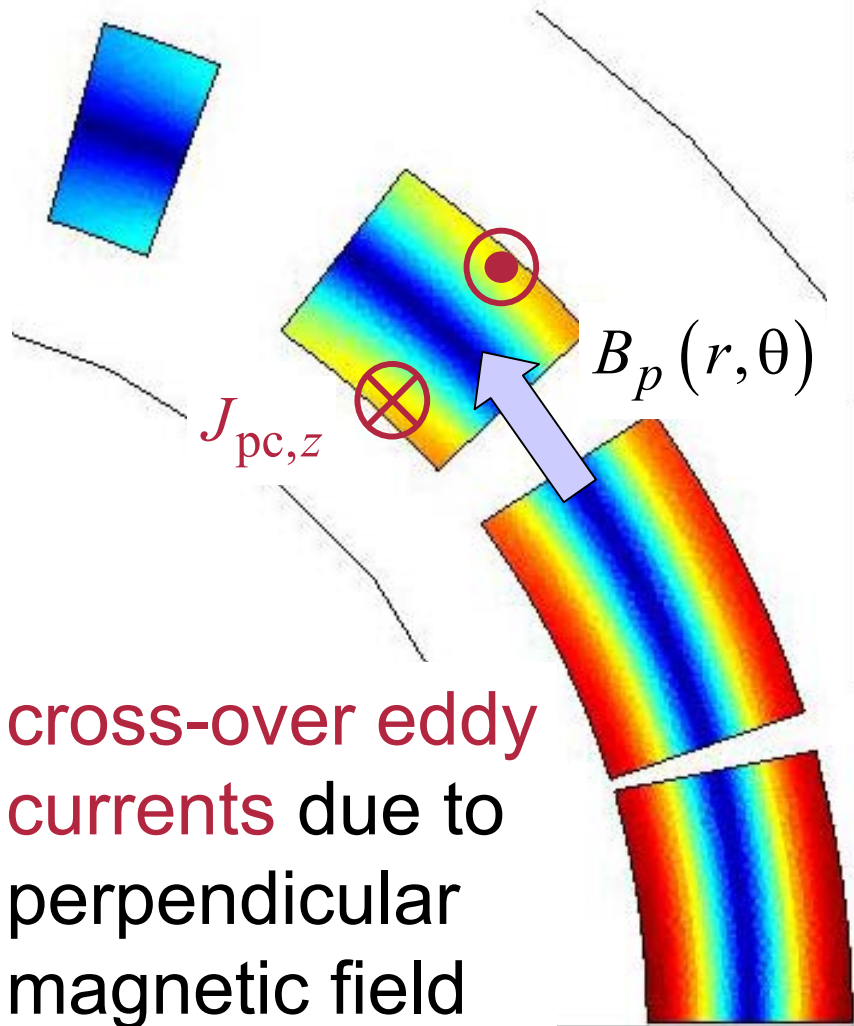

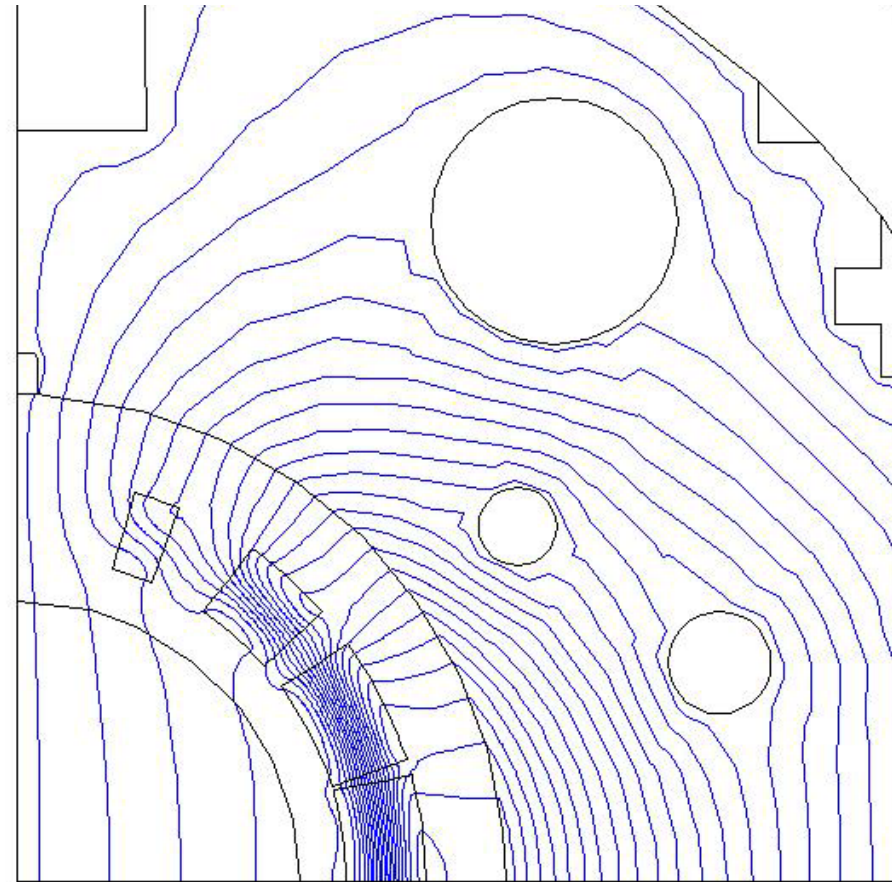cross-over eddy currents due to perpendicular magnetic field



cross-over magnetisation

- hybrid method for circuit analysis
 - ➔ *convenient field-circuit modelling*
- solution of the coupled algebraic systems of equations
- specialised conductor models
 - ➔ *complicated eddy current phenomena*
- applications to
 - ◆ electrical machine
 - ◆ foil winding transformer
 - ◆ superconductive magnets, Rutherford cable